

MOS VLSI PROJECT

5 BIT CARRY LOOK AHEAD ADDER


BY

K Ram Mohan (2021VST9509)


Abhinav Reddy (1190455)

P Reddy Sai Gagan (2022EEE2022)

SCHEMATIC AND LOGIC WORKING DIAGRAMS:

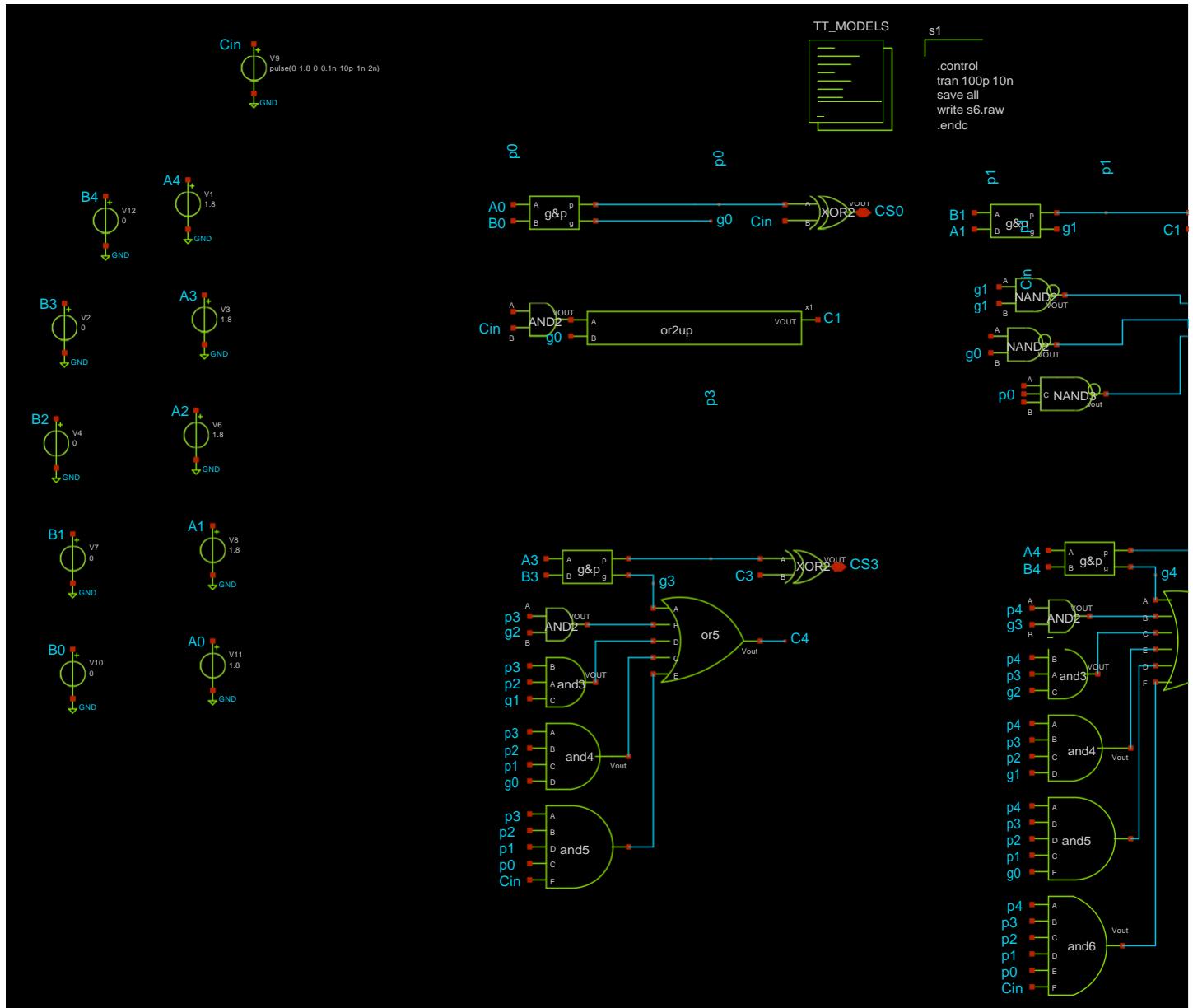

LOGIC WORKING DIAGRAMS:

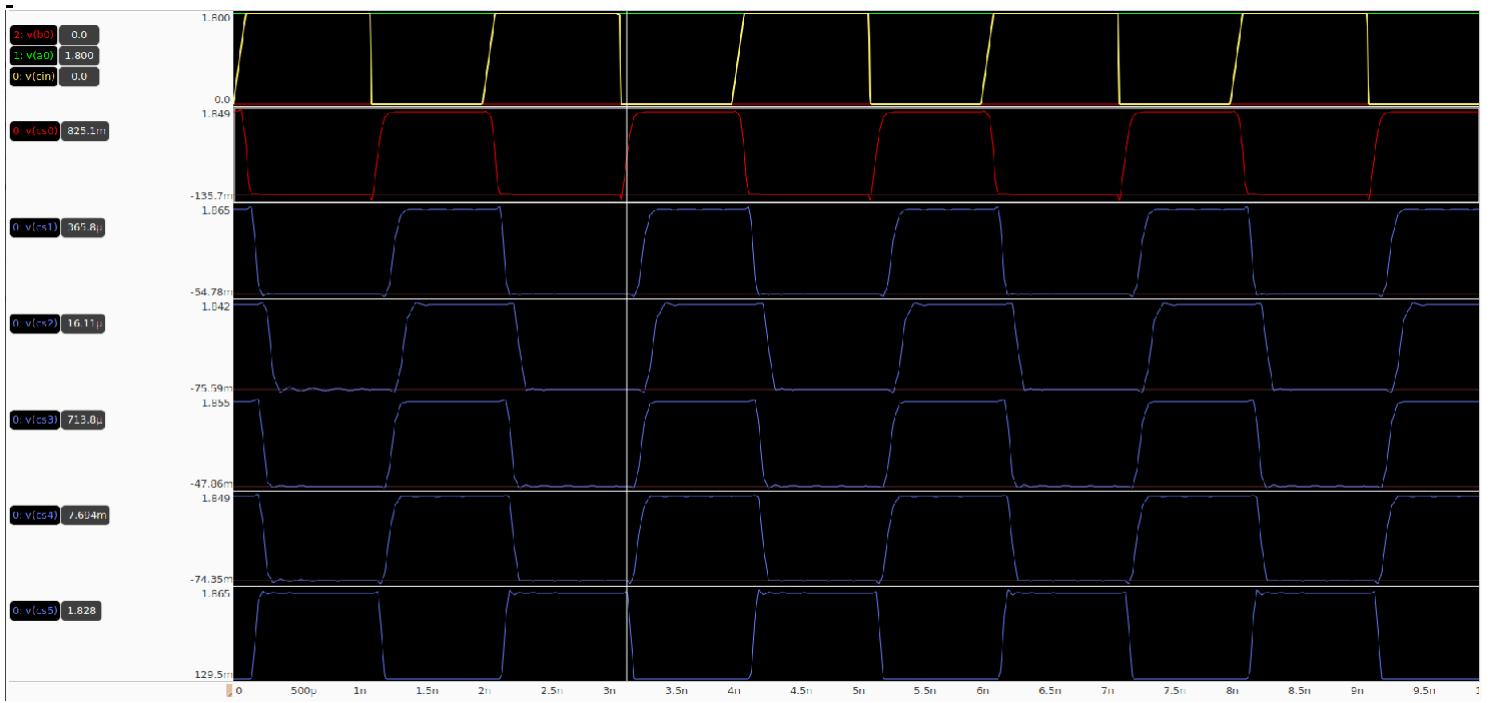

WHAT DID WE TRY:

We have implemented 5 bit adder using ripple adder architecture which resulted in large delays. so we have tried carrylook ahead adder which resulted in lesser delay than ripple adder architecture . we have designed all basic gates like AND(2-6 input),nor(2-6),OR(2-6),XOR 2 as shown in the above schematic diagram. We used PSEUDO NOR'S to minimize further more delay.

LIMITATIONS:

Width of any gate can't be less twice of the technology width parameter, whenever we tried we got errors and also width tradeoff should be take care as more width also creates delay increase. We got more delay using NAND gates so we avoided AND gates directly from static CMOS logic gate.

THEORY ON CARRY LOOK AHEAD ADDER:

A carry-Look ahead adder is a fast parallel adder as it reduces the propagation delay by more complex hardware, hence it is costlier. In this design, the carry logic over fixed groups of bits of the adder is reduced to two-level logic, which is nothing but a transformation of the ripple carry design.

This method makes use of logic gates so as to look at the lower order bits of the augend and addend to see whether a higher order carry is to be generated or not

The operation of carry look ahead is based on two scenarios:

Calculate every digit position to know whether that position is propagating a carry bit that comes from its right position.

Then combine the calculated values to produce the output for every set of digits where the group generates a propagation bit that comes from the right position.

Carry look ahead adders operate by generating two bits called Carry Propagate and Carry Generate which are represented by Cp and Cg. The Cp bit gets propagated to the next stage and the Cg bit is used for generating the output carry bit and this is independent of the input carry bit.

CRITICAL PATH:

Total delay of CLA=(delay of the generate/propagate gates)+(total delay of the k-bit blocks) + (No. of carry look ahead adder blocks × total delay of the carry look ahead blocks from Cin to Cout) + (No. of ripple carry adder blocks × delay of a ripple carry adder)
 Total delay of CLA=(delay of the generate/propagate gates)+(total delay of the k-bit blocks) + (No. of carry look ahead adder blocks × total delay of the carry look ahead blocks from Cin to Cout) + (No. of ripple carry adder blocks × delay of a ripple carry adder)

Substituting the terms we get, 01-10-2022

$$t_{CLA} = t_{pg} + t_{pg_block} + (Nk - 1).t_{AND_OR} + k.T_{fa}$$


input -> S4 is the critical path.

Critical path is from input -> generator propagate block -> AND blocks -> carry of (n-1)th bit -> final sum block of final bit


SCHEMATIC SIMULATIONS ACROSS ALL CORNERS (TT,SS,FS,SF,FF) AND TEMPERATURES(-40,27,125):

TT corner - Temperature - (-40)
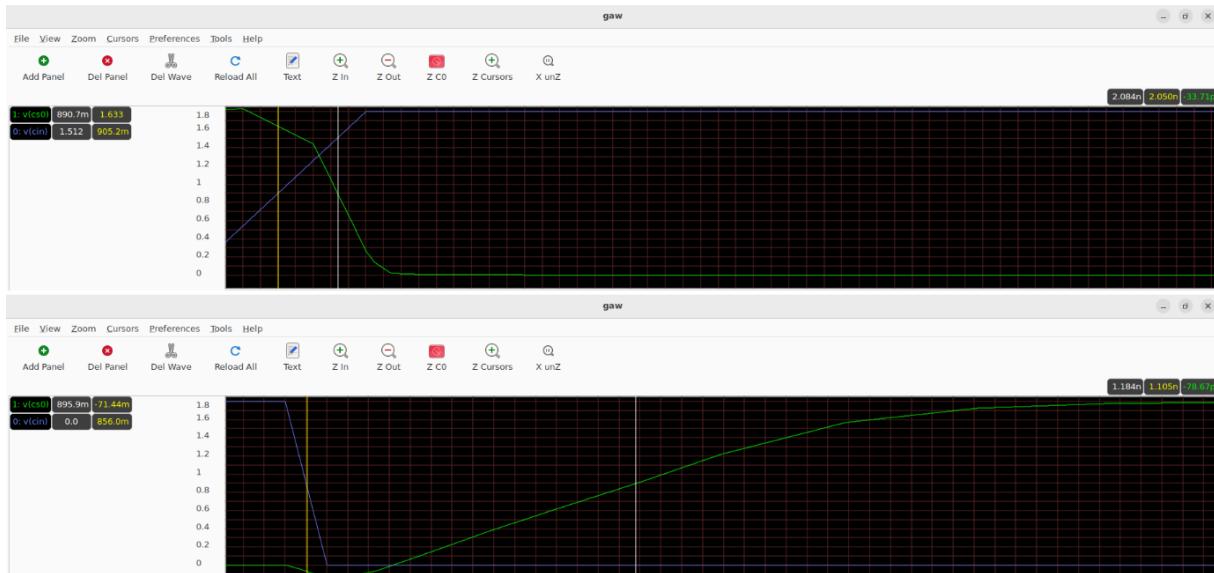
$$S0 \text{ delay} = (33.71 + 78.67)/2 = 56.19 \text{ p}$$


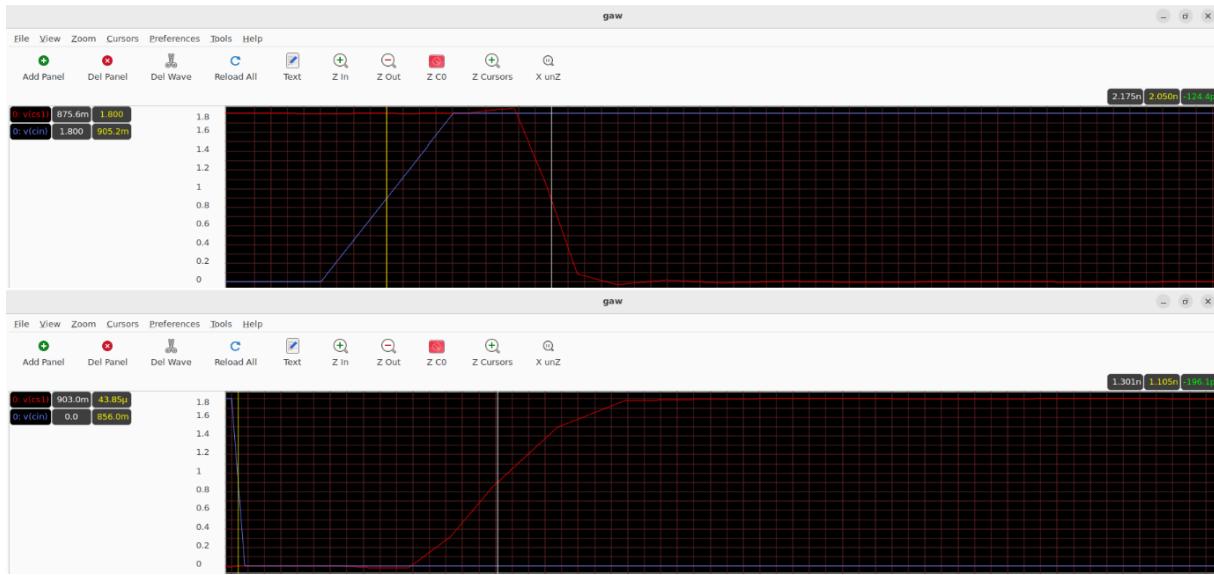
$$S1 \text{ - delay} = (196 + 124)/2 = 160 \text{ p}$$




$$S2 \text{ delay} = (259 + 291) / 2 = 271$$





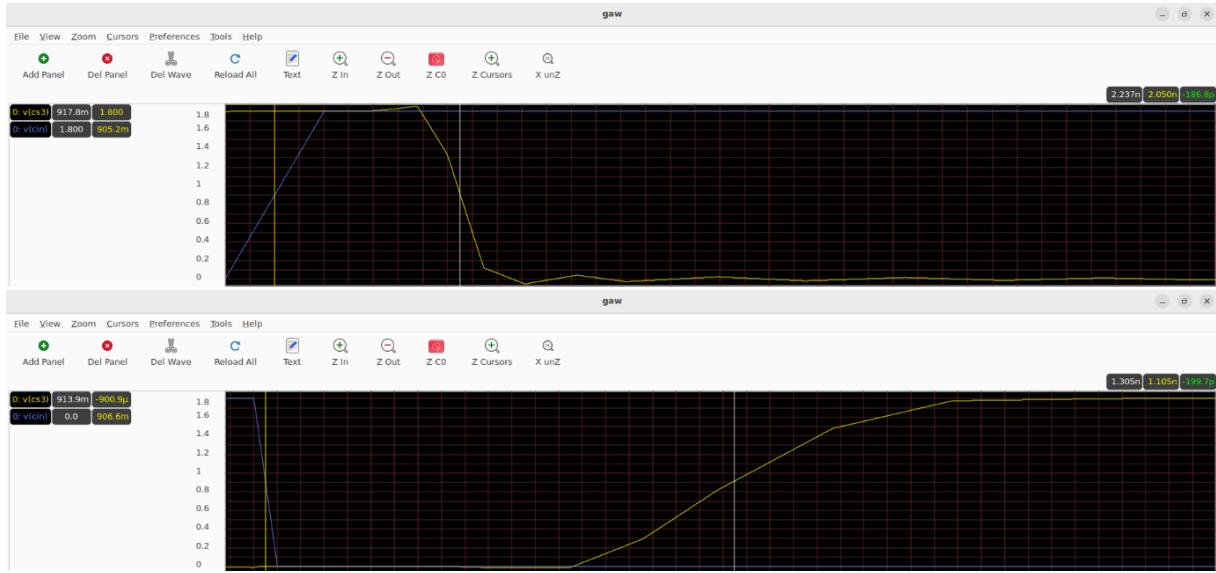
$$S3 \text{ delay} = (186+199)/2 = 192.5\text{p}$$



$$S4 \text{ delay} = (194+171)/2 = 182.5\text{p}$$


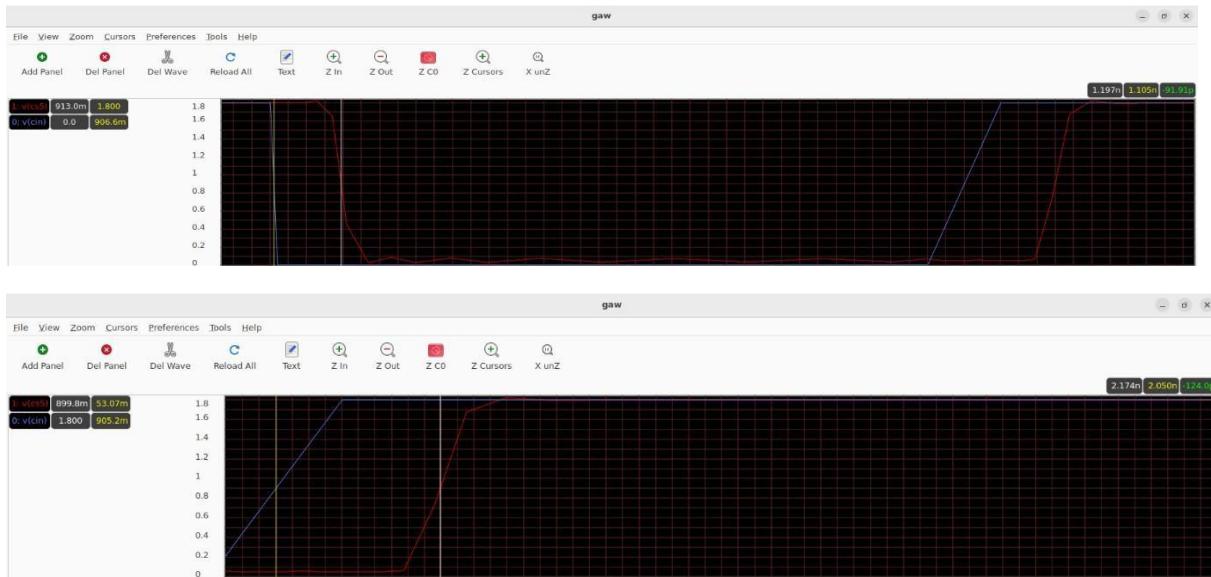
$$S5 \text{ delay} = (91+124)/2 = 107.5\text{p}$$





TT corner – Temperature (27)

$$S0 \text{ delay} = (37.13 + 74.59)/2 = 56\text{p}$$


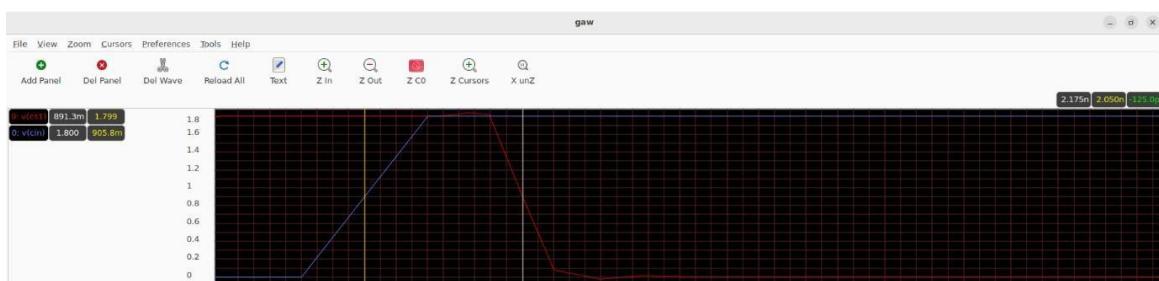
$$S1 \text{ delay} = (125 + 199)/2 = 162\text{p}$$





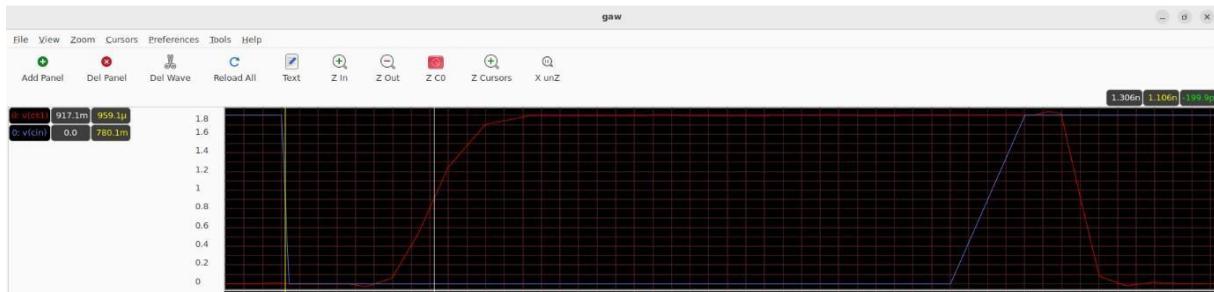

$$S2 \text{ delay} = (252 + 284)/2 = 268\text{p}$$




$$S3 \text{ delay} = (185+195)/2 = 190$$

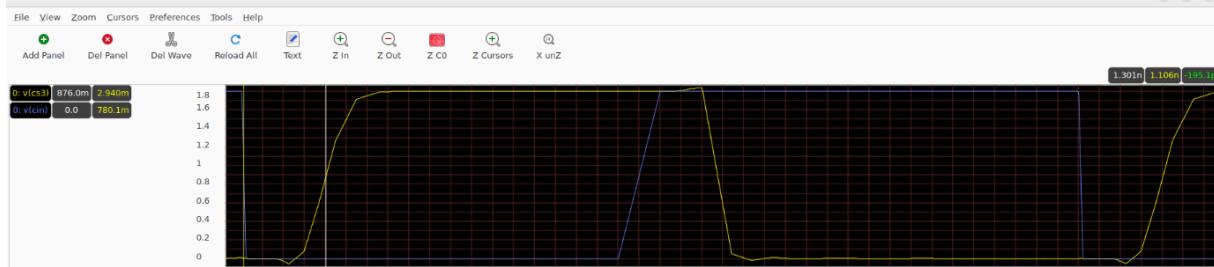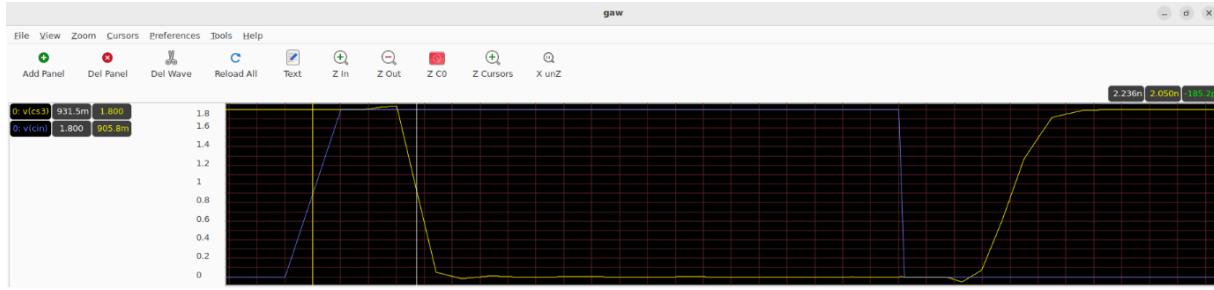

$$S4 \text{ delay} = (202+167)/2 = 184.5\text{p}$$



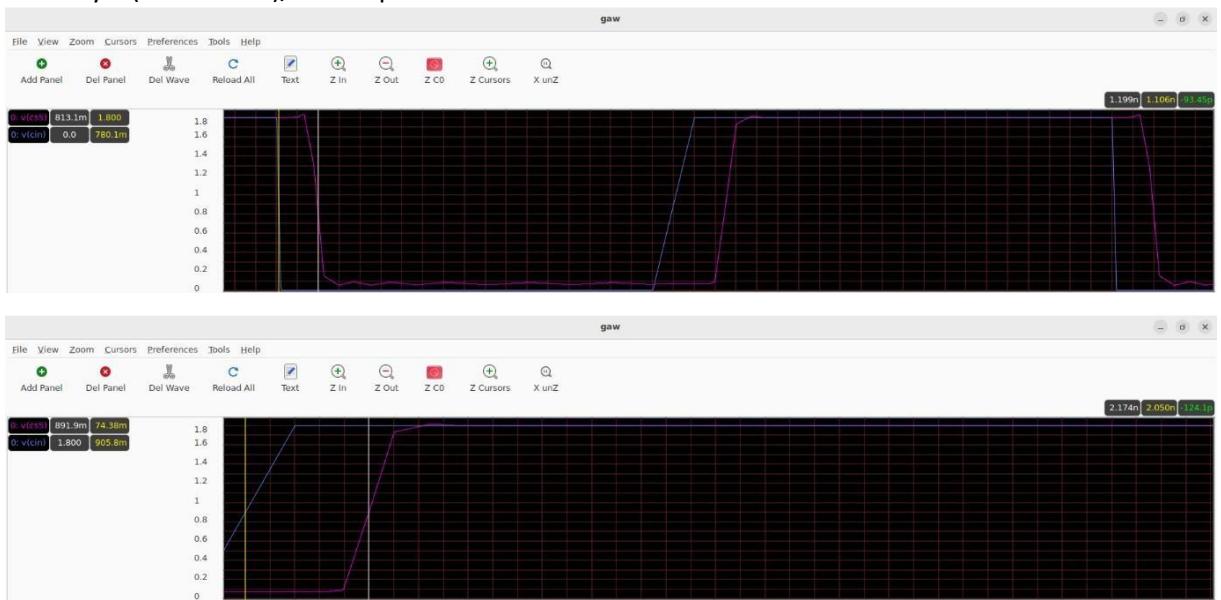
$$S5 \text{ delay} = (93.45 + 124)/2 = 109\text{p}$$





TT corner – Temperature (125)
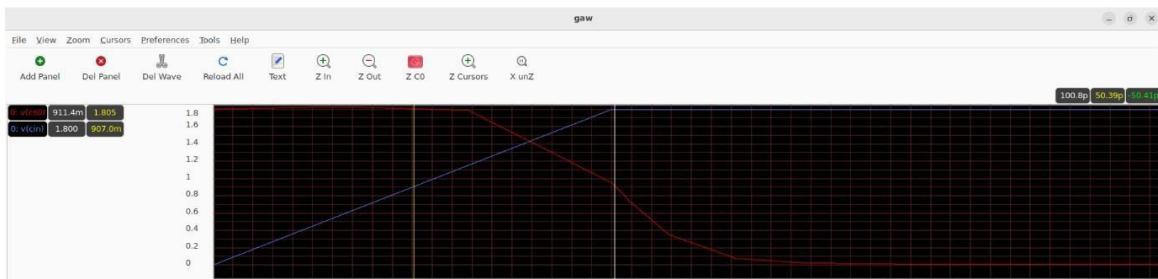
$$S0 \text{ delay} = (50 + 69)/2 = 59.5$$







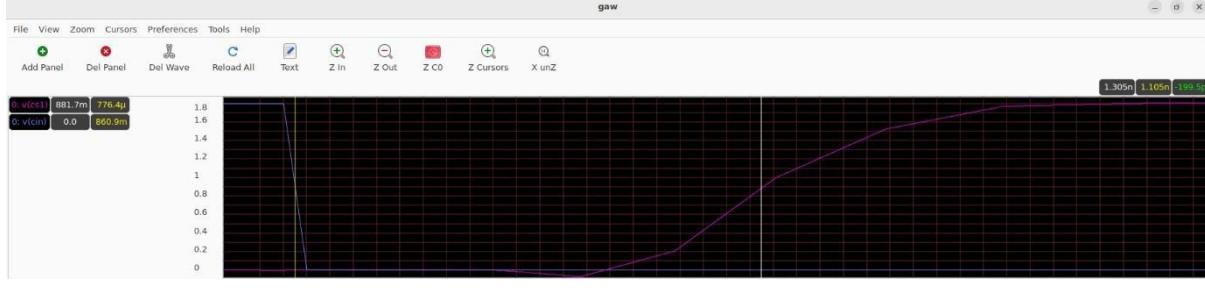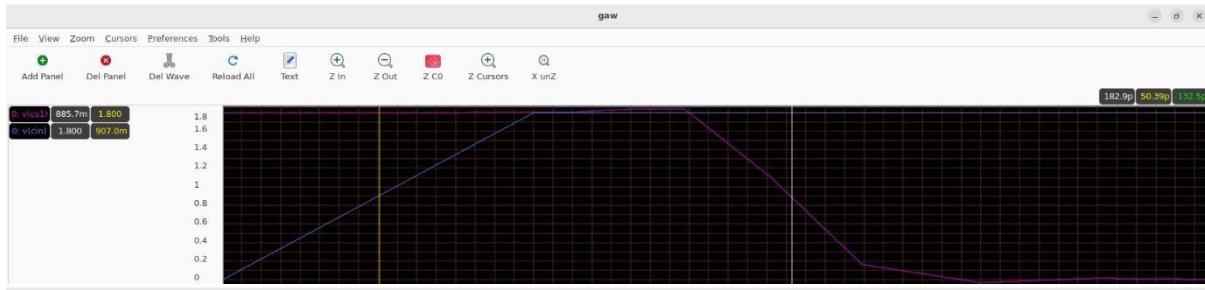
$$S1 \text{ delay} = (132 + 199)/2 = 166\text{p}$$



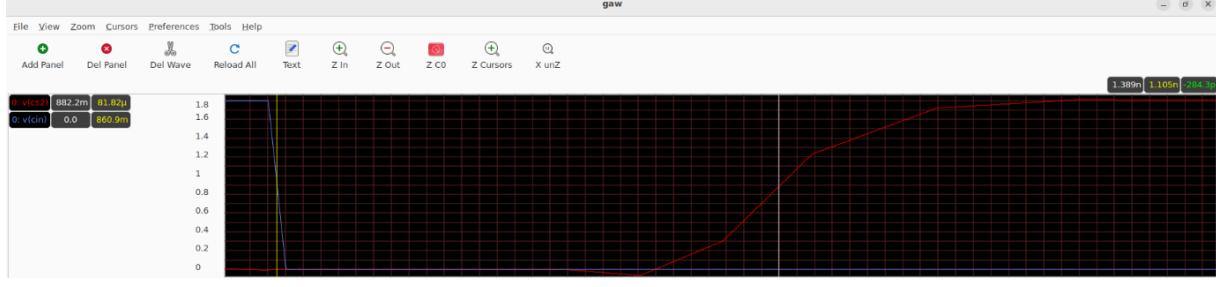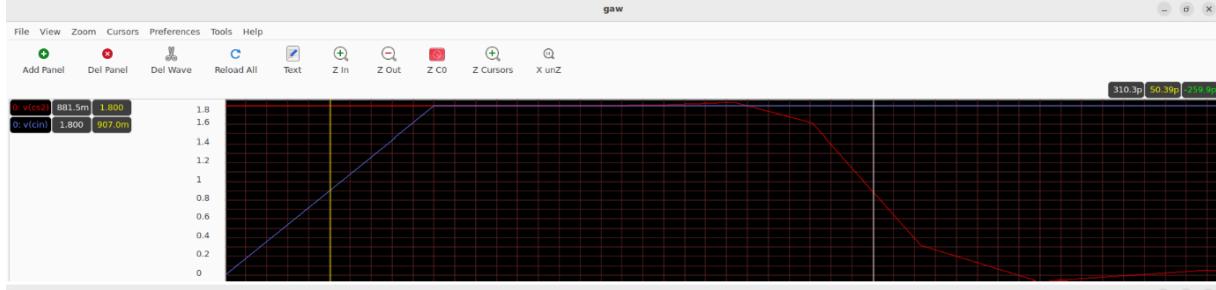
$$S2 \text{ delay} = (259 + 284)/2 = 271.5\text{p}$$


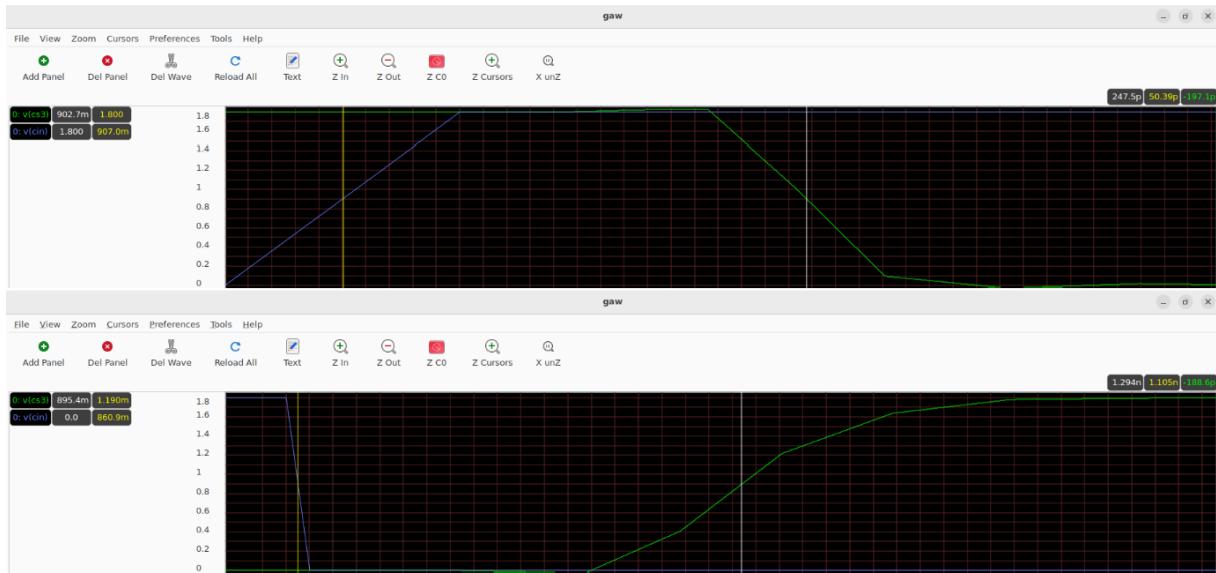
$$S3 \text{ delay} = (197 + 188)/2 = 192.5 \text{ p}$$



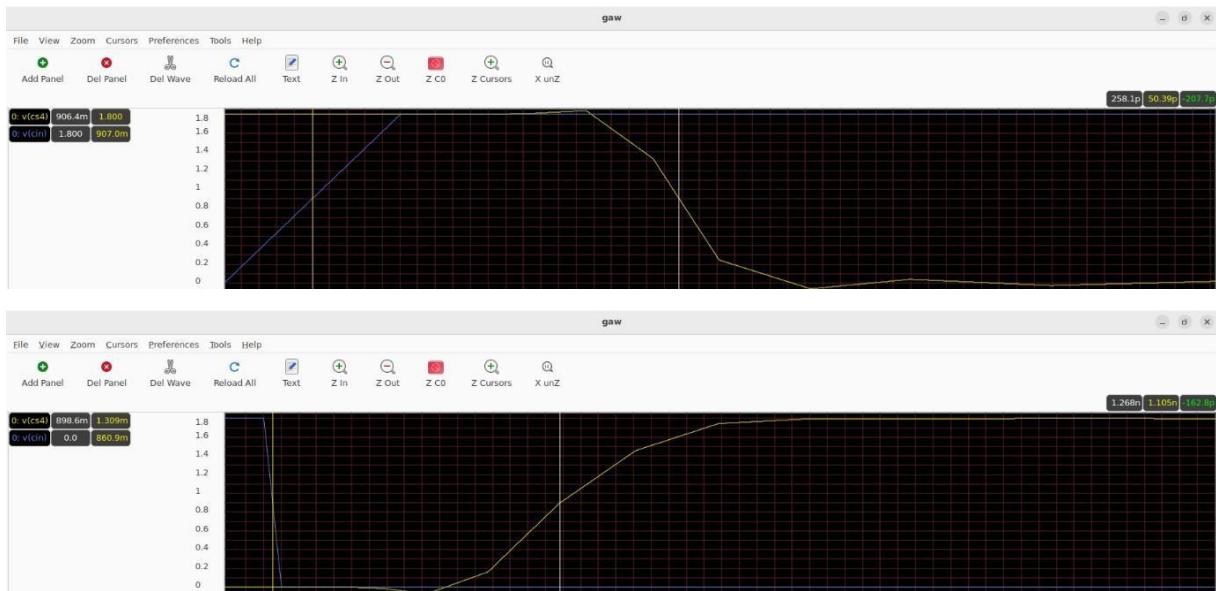
$$S4 \text{ delay} = (207+162)/2 = 184.5\text{p}$$



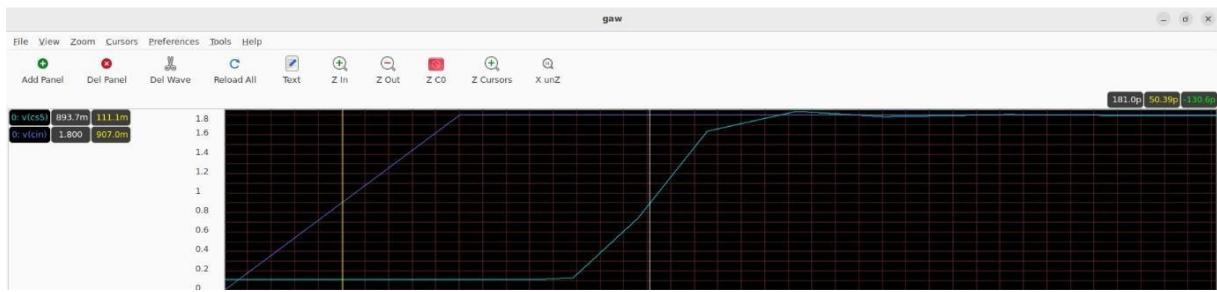
$$S5 \text{ delay} = (89+130)/2 = 109.5\text{p}$$






SS corner –Temperature (-40)

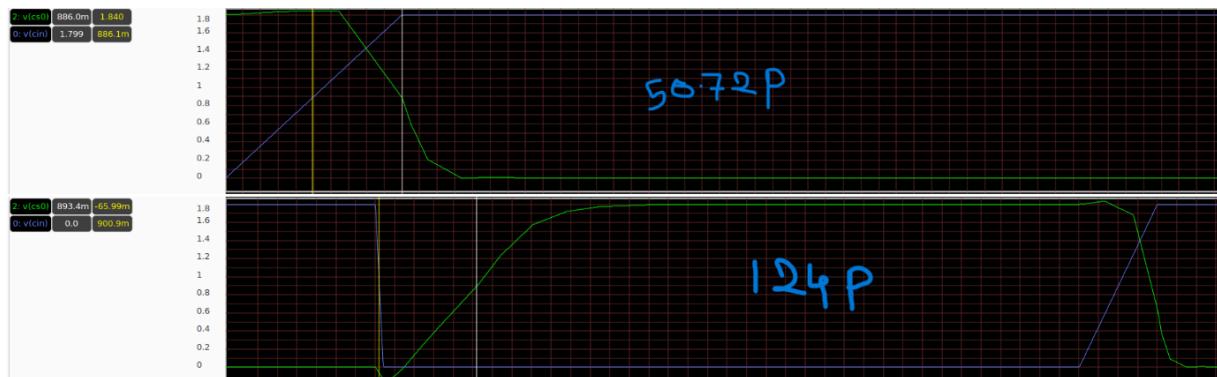
$$S_0 \text{ delay} = (50.72 + 124)/2 = 87 \text{ p}$$



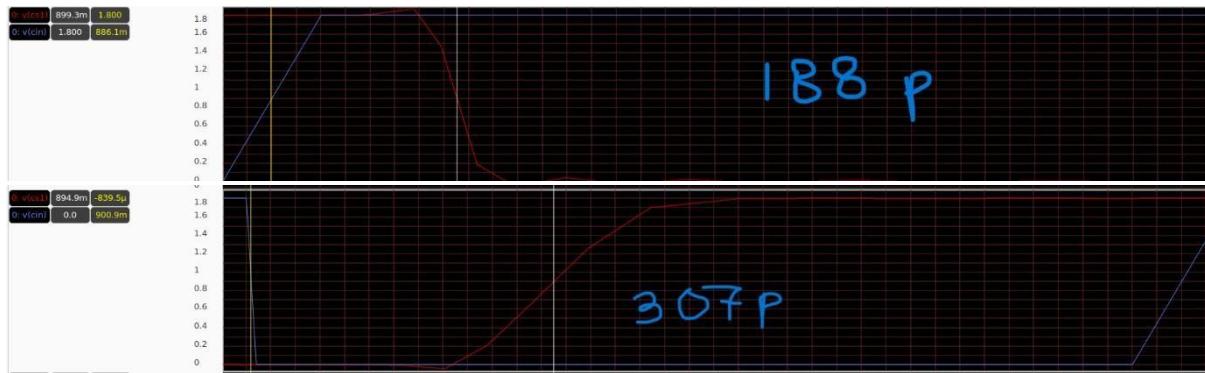
$$S_1 \text{ delay} = (188 + 307)/2 = 247.5 \text{ p}$$



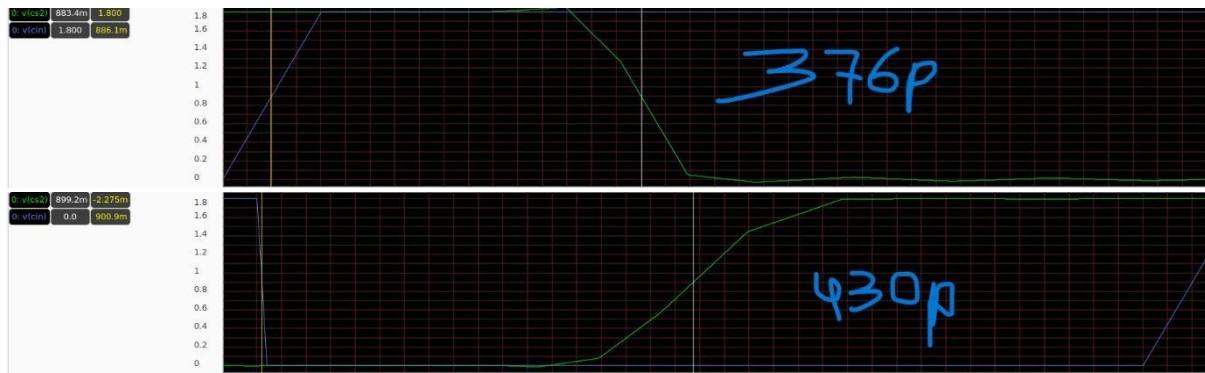
$$S_2 \text{ delay} = (376 + 430)/2 = 388 \text{ p}$$



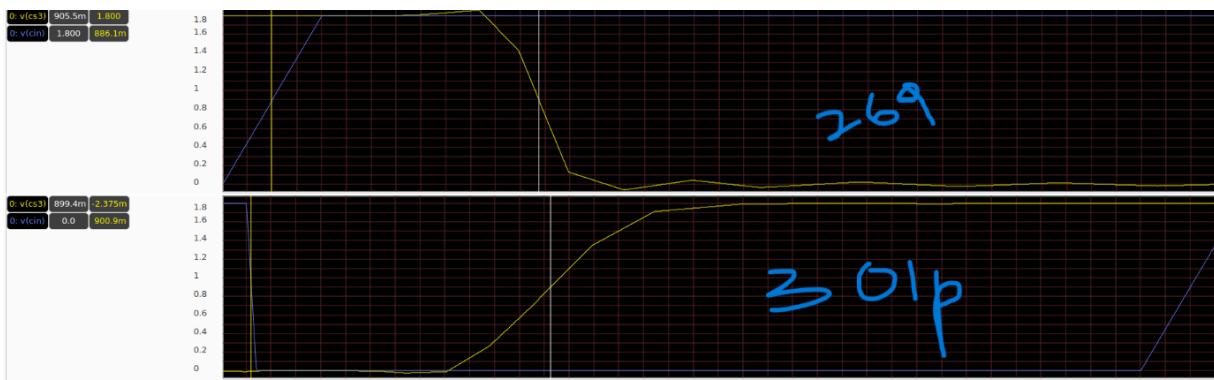
$$S_3 \text{ delay} = (269 + 301)/2 = 285 \text{ p}$$


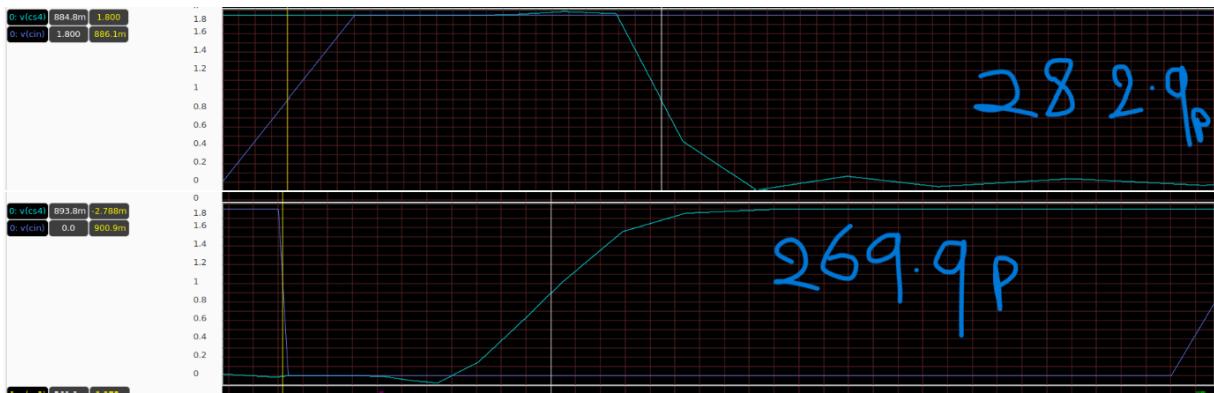
$$S4 \text{ delay} = (282.9 + 269.9)/2 = 277\text{p}$$




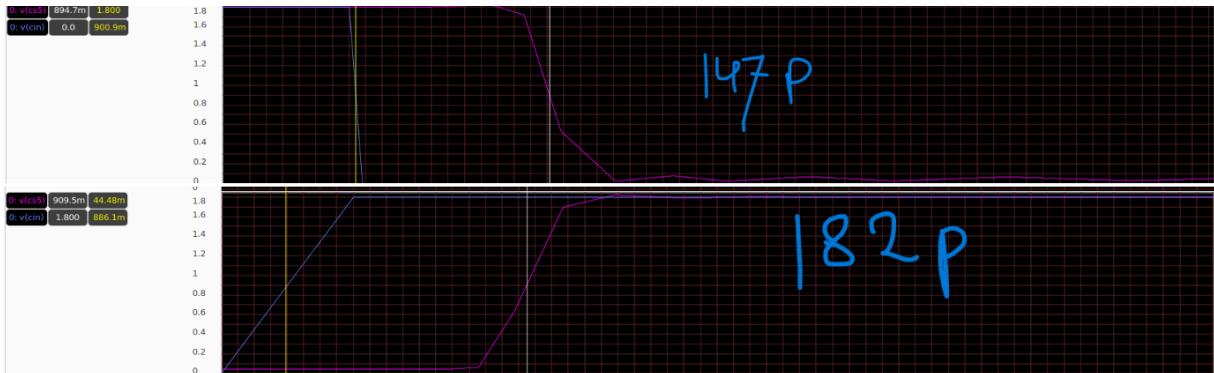
$$S5 \text{ delay} = (147+182)/2 = 164.5\text{ P}$$




SS CORNER – TEMPERATURE (27)
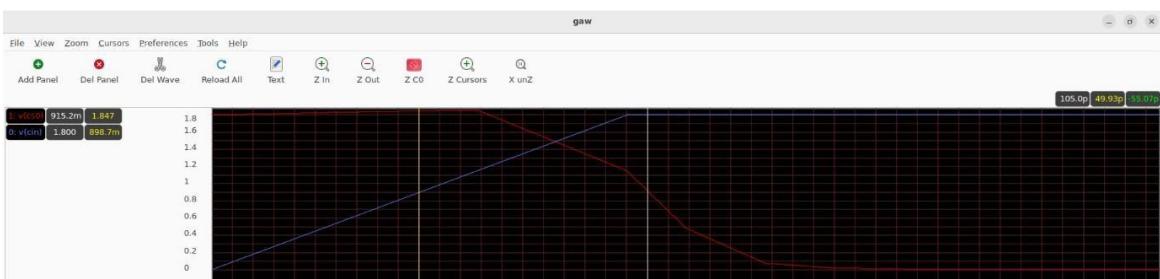
$$S0 \text{ delay} = (55+114)/2 = 84.5\text{ p}$$




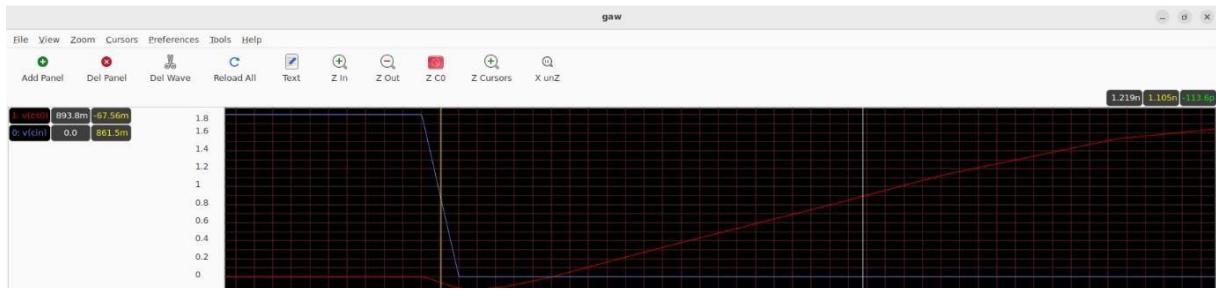
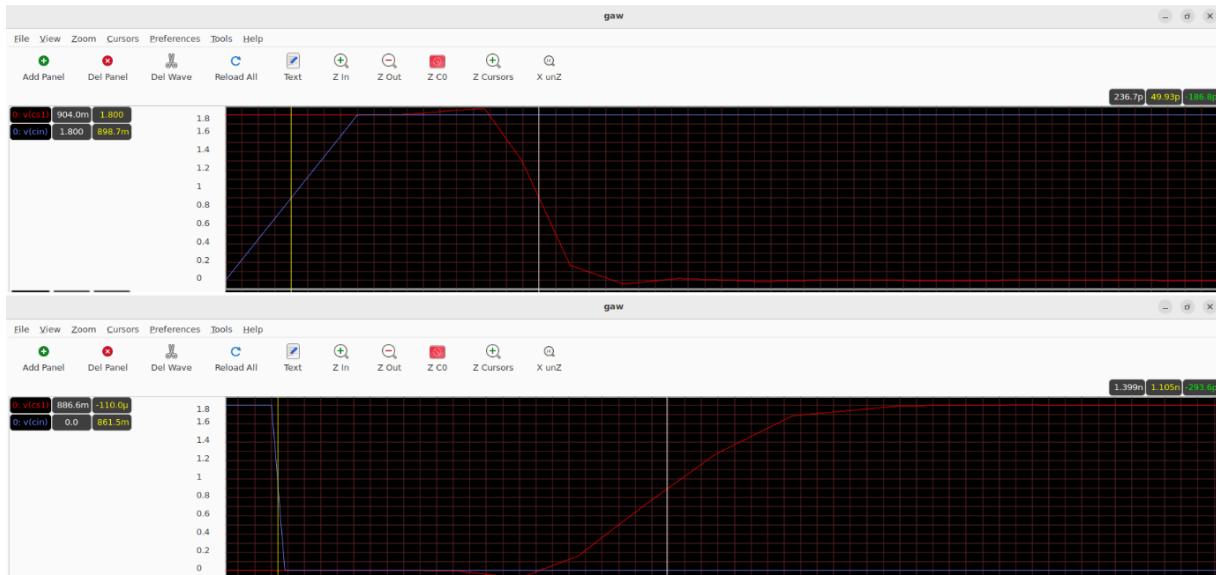
$$S1 \text{ delay} = (186+294)/2 = 240\text{p}$$




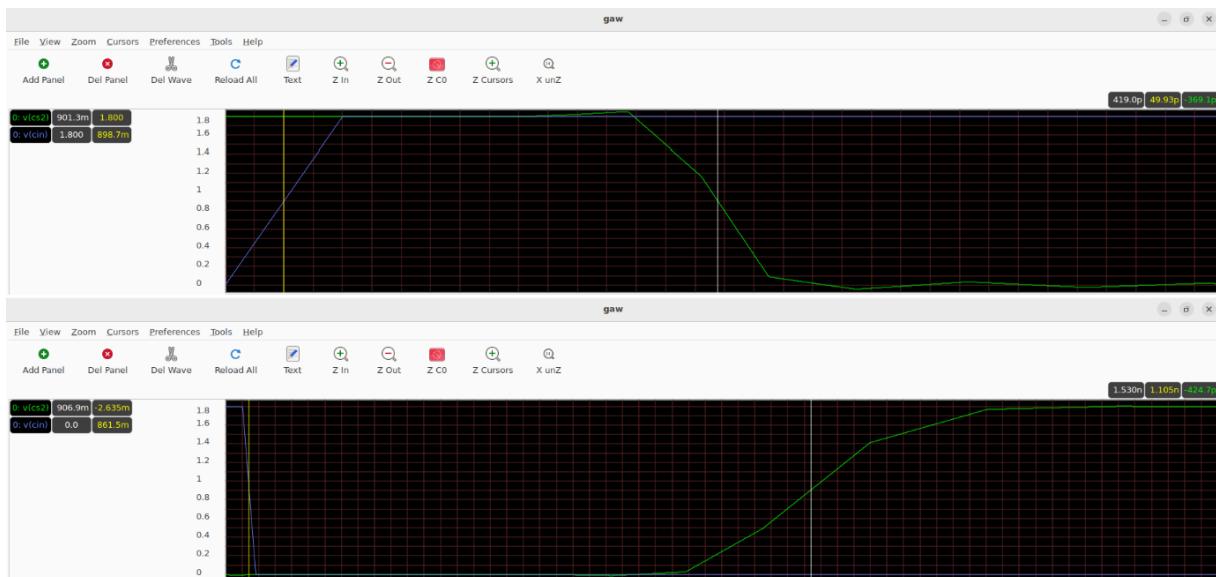
$$S2 \text{ delay} = (369+424)/2 = 396.5\text{p}$$




$$S3 \text{ delay} = (270+283)/2 = 276.5\text{ p}$$


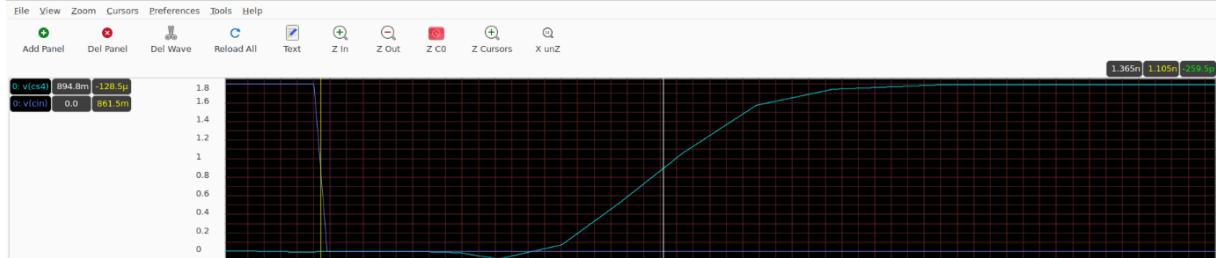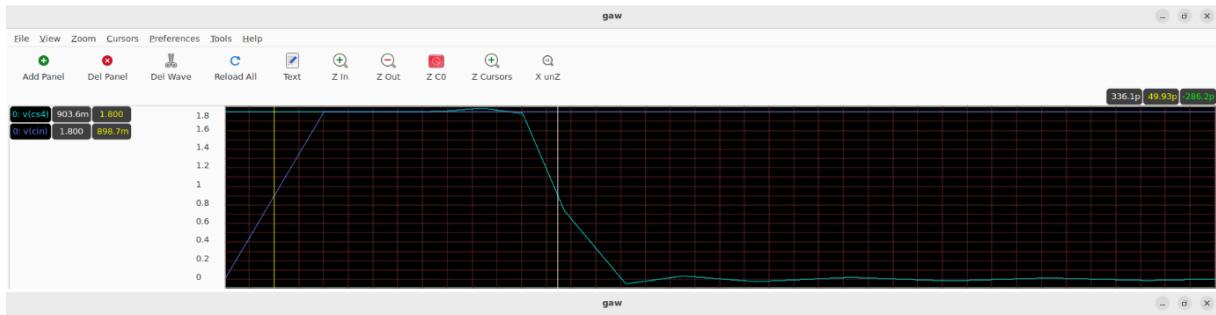
$$S4 \text{ delay} = (286+259)/2 = 272.5 \text{ p}$$



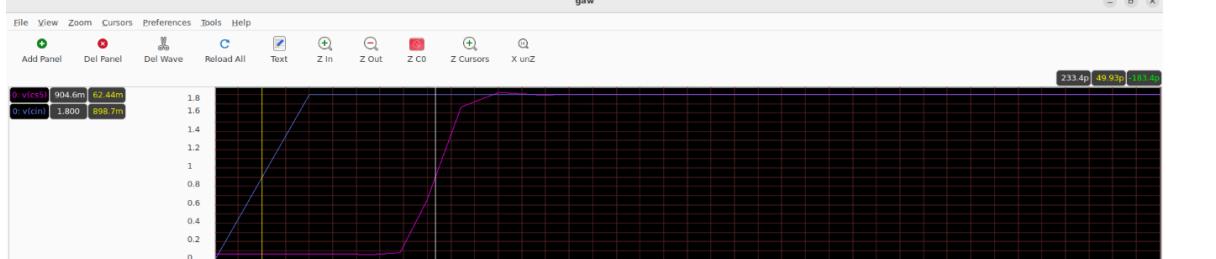
$$S5 \text{ delay} = (139+183)/2 = 161\text{p}$$




SS corner – Temperature (125)

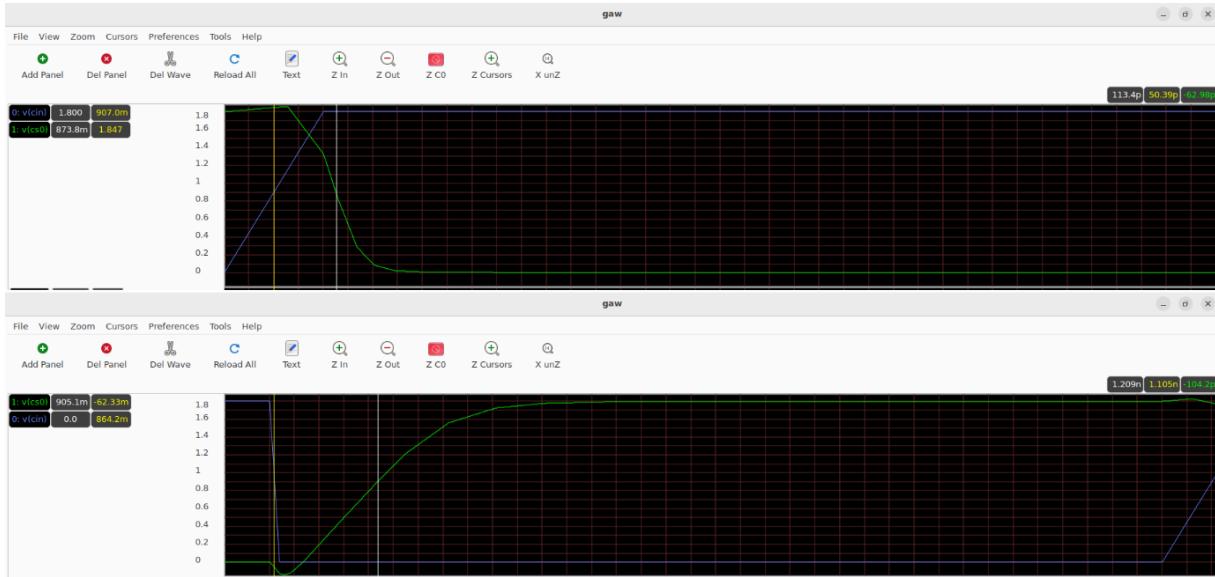
$$S1 \text{ delay} = (63+104)/2 = 83.5\text{p}$$


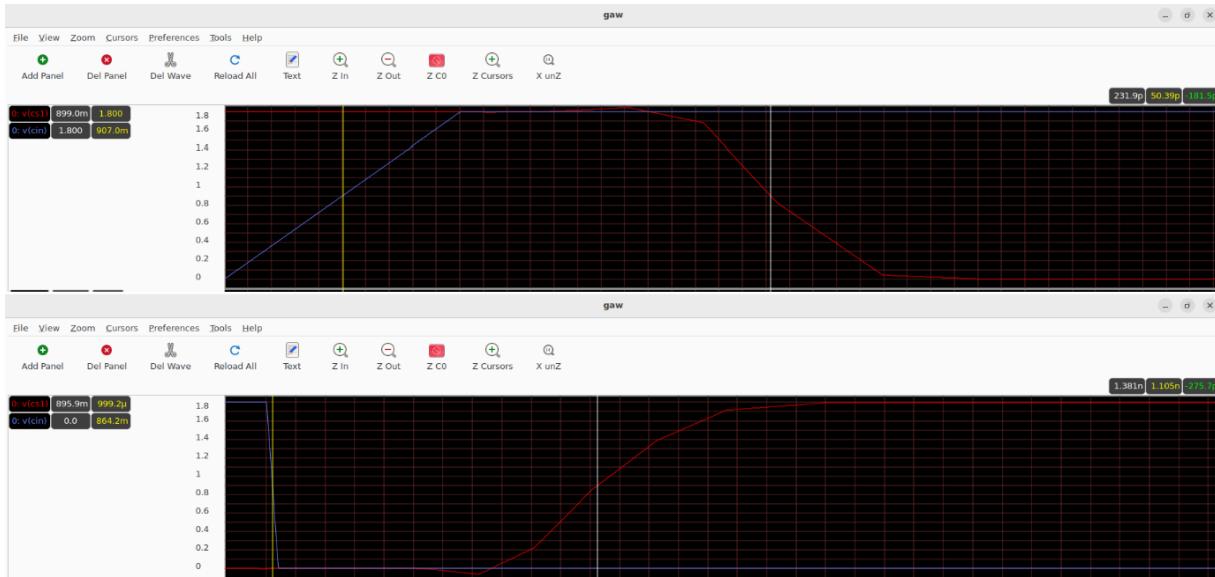
$$S1 \text{ delay} = (182+275)/2 = 228\text{p}$$



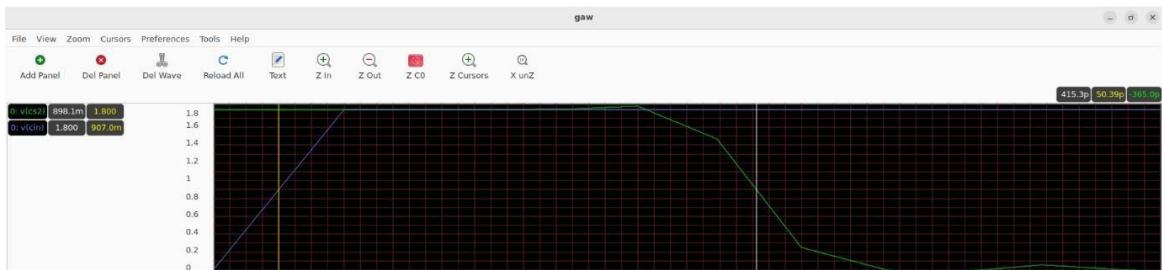
$$S2 \text{ delay} = (365 + 414)/2 = 389.5\text{p}$$







S3 delay = $(278+263)/2 = 268\text{p}$

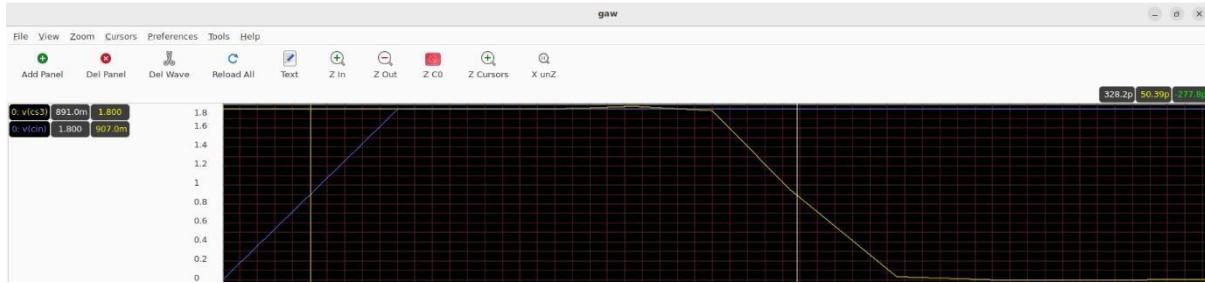

S4 delay = $(299+239)/2 = 269\text{p}$

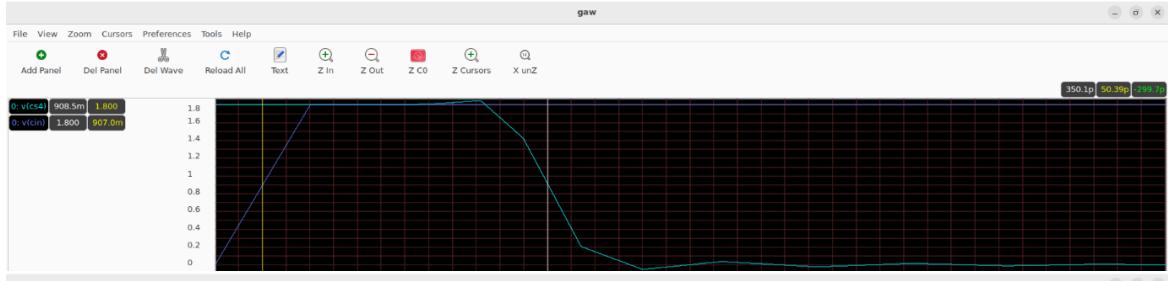

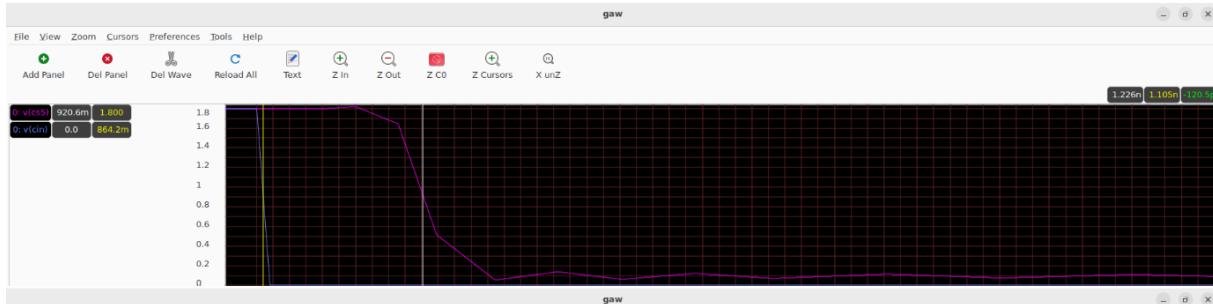
$$S5 \text{ delay} = (120+187)/2 = 153.5\text{p}$$




$$FS \text{ corner - Temperature (125)} \quad SO \text{ delay} = (63.4+57.6)/2 = 60.5\text{p}$$




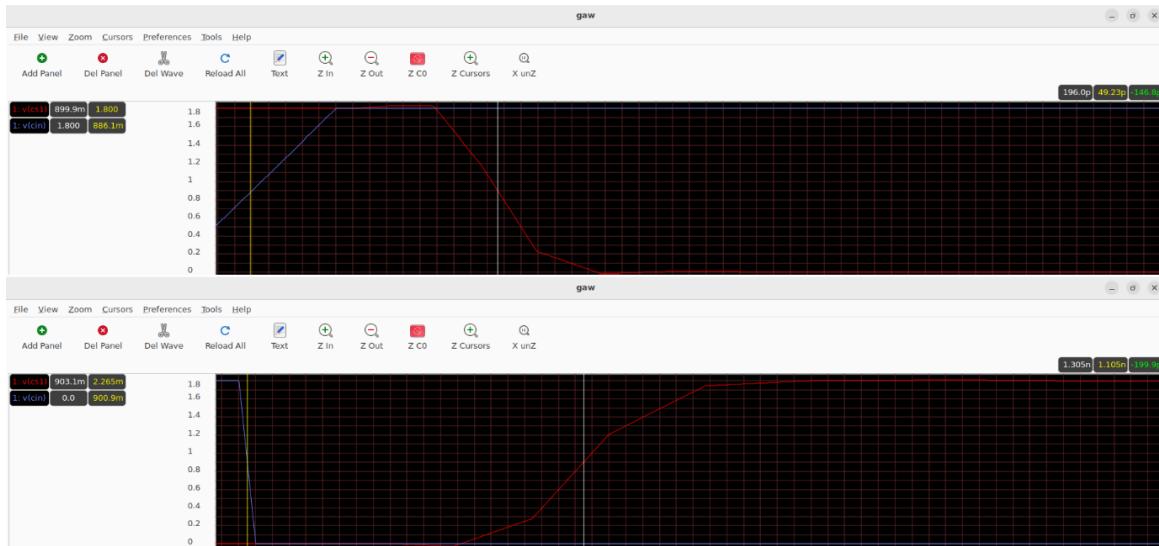
$$S1 \text{ delay} = (146+200)/2 = 173\text{p}$$



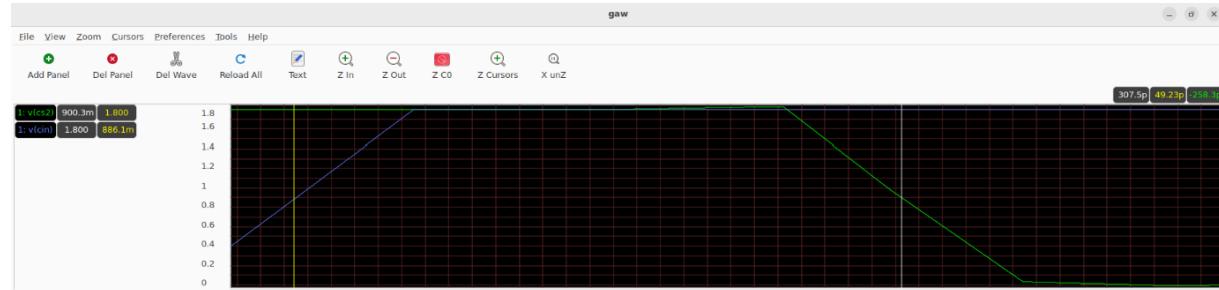
$$S2 \text{ delay} = (258+251)/2 = 254.5\text{p}$$




$$S3 \text{ delay} = (195+187)/2 = 191$$

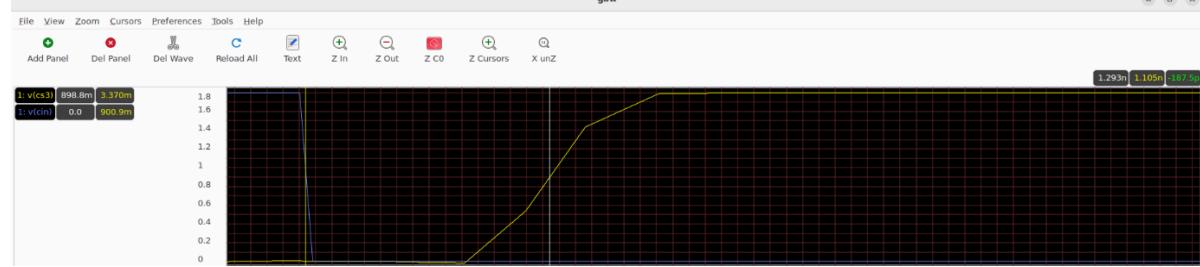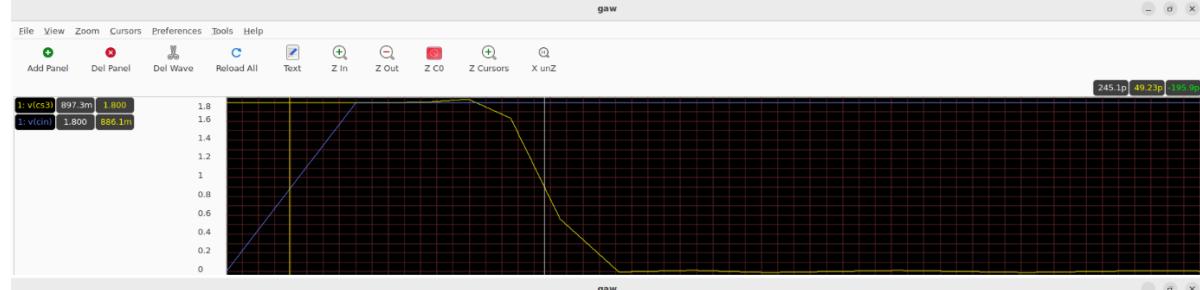
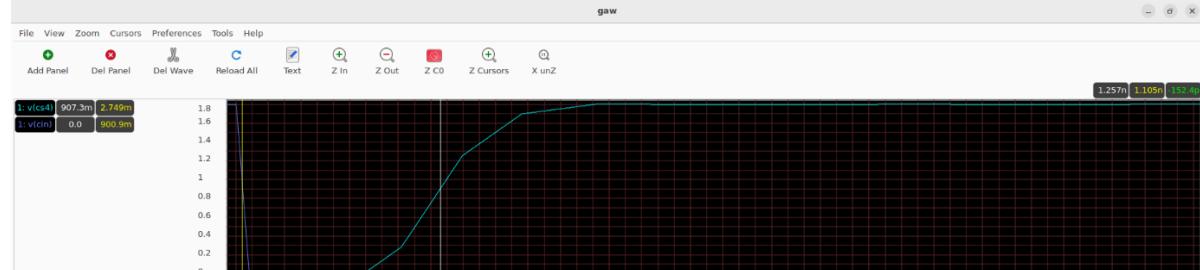
$$S4 \text{ delay} = (207+152)/2 = 179.5\text{p}$$


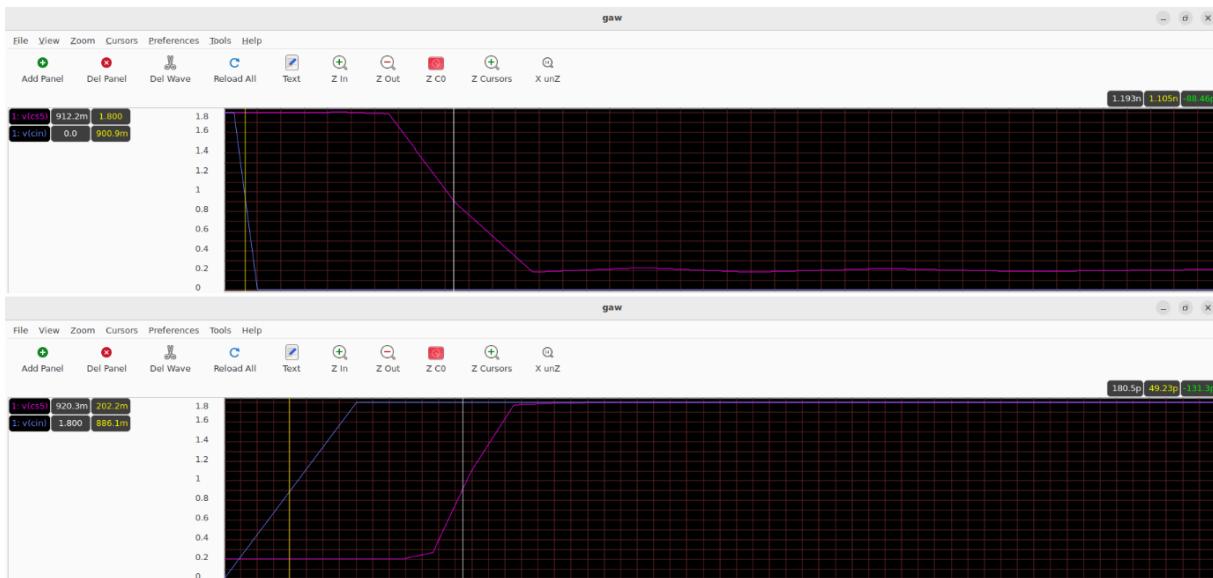
$$S5 \text{ delay} = (88+131)/2 = 109.5 \text{ p}$$





FS corner – temperature (-40)

$$S0 \text{ delay} = (56.64+56.42)/2 = 56.5$$




$$S1 \text{ delay} = (130+178)/2 = 154$$


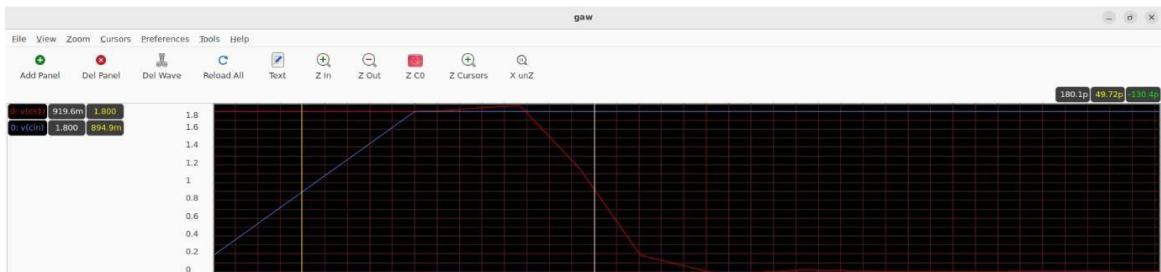


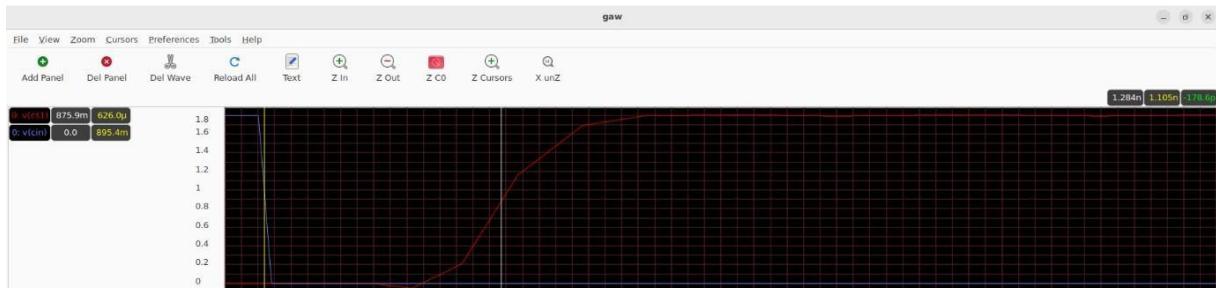


$$S2 \text{ delay} = (249+259)/2 = 254$$

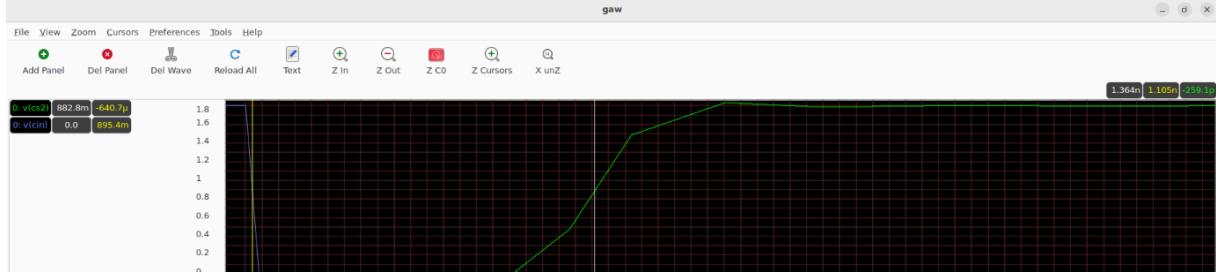
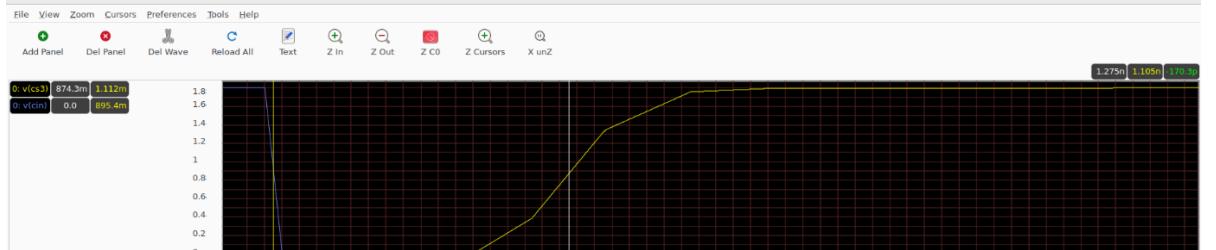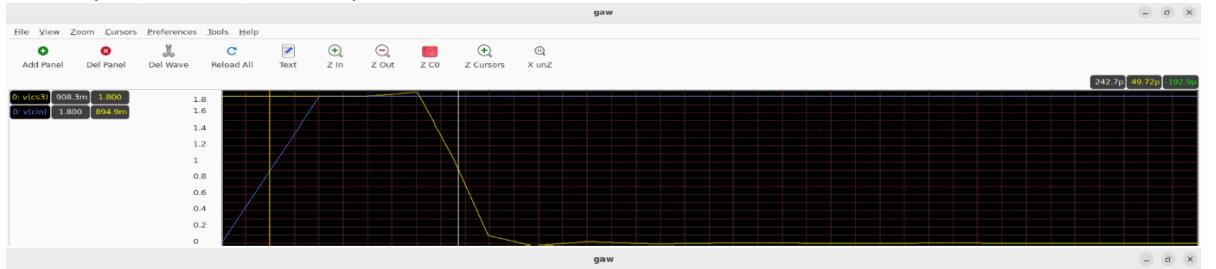
$$S3 \text{ delay} = (192+170)/2 = 181p$$



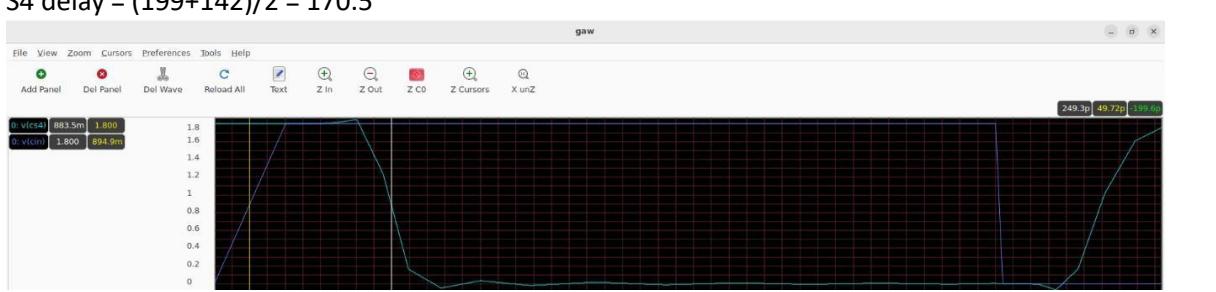
$$S4 \text{ delay} = (199+142)/2 = 170.5$$




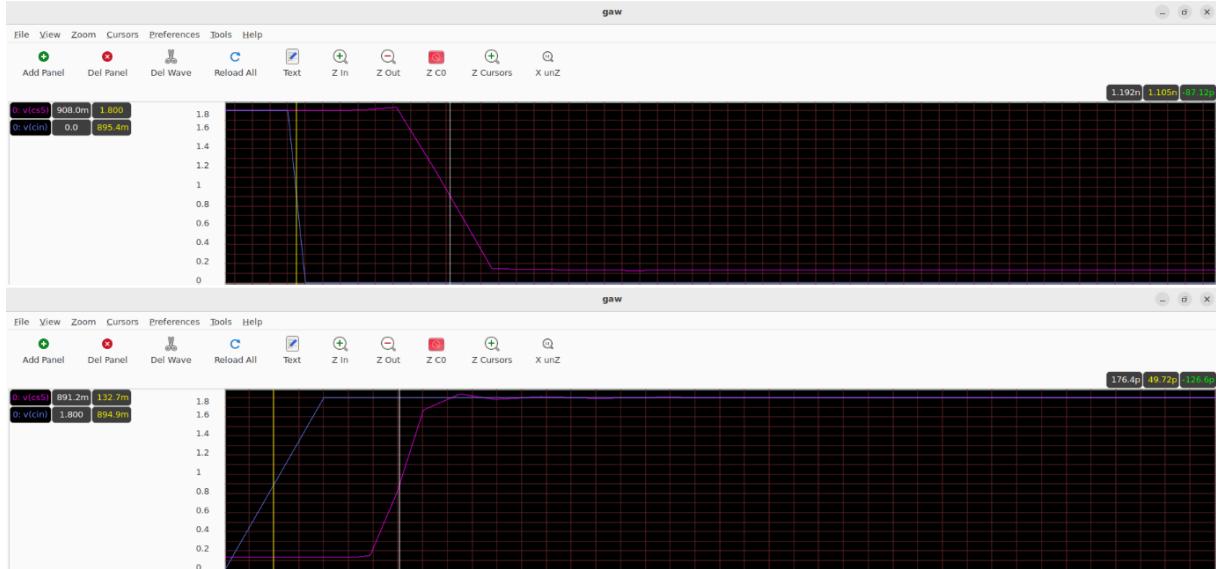
$$S5 \text{ delay} = (87+126)/2 = 150\text{p}$$



FS corner – Temperature (27)


$$S0 \text{ delay} = (56.85+55.83)/2 = 56.34$$




$$S1 \text{ delay} = (131.1+179.5)/2 = 155.3 \text{ p}$$


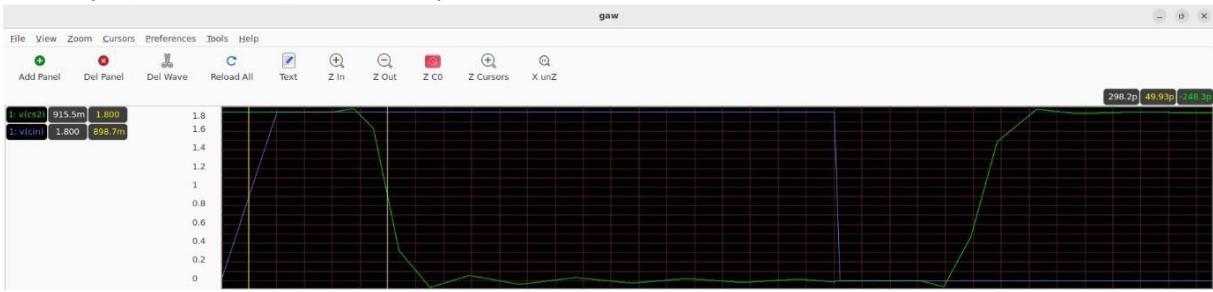
$$S2 \text{ delay} = (248.3 + 259.6)/2 = 253.95 \text{ p}$$



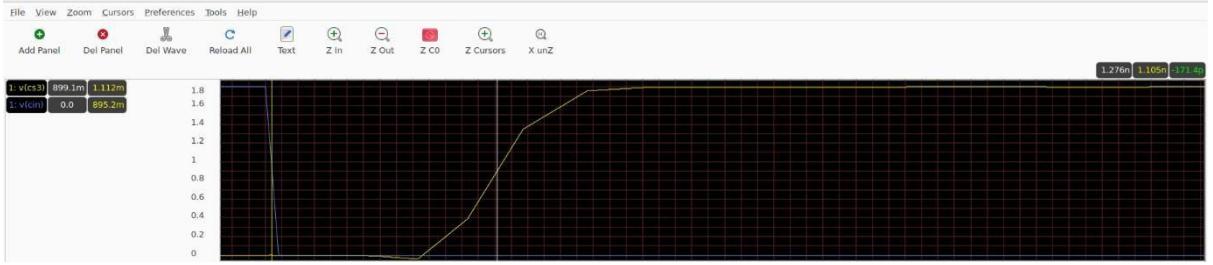
$$S3 \text{ delay} = (193.7 + 171.4)/2 = 182.5 \text{ p}$$



$$S4 \text{ delay} = (198+143)/2 = 170.5\mu$$



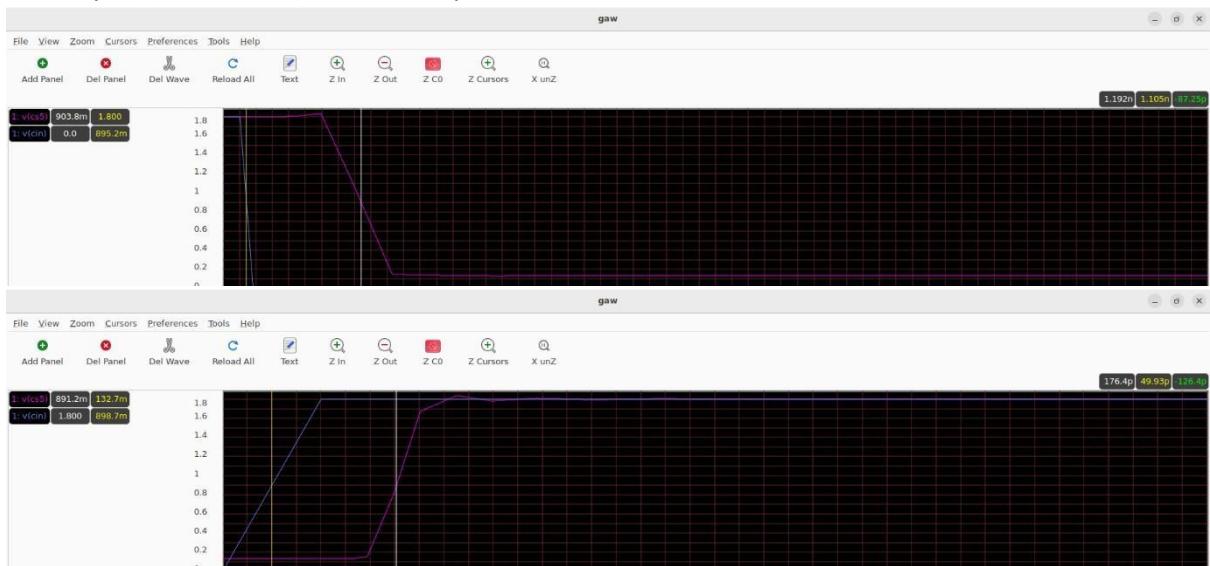
$$S5 \text{ delay} = (87.25+126.4)/2 = 106.825\mu$$




SF corner Temperature (27)

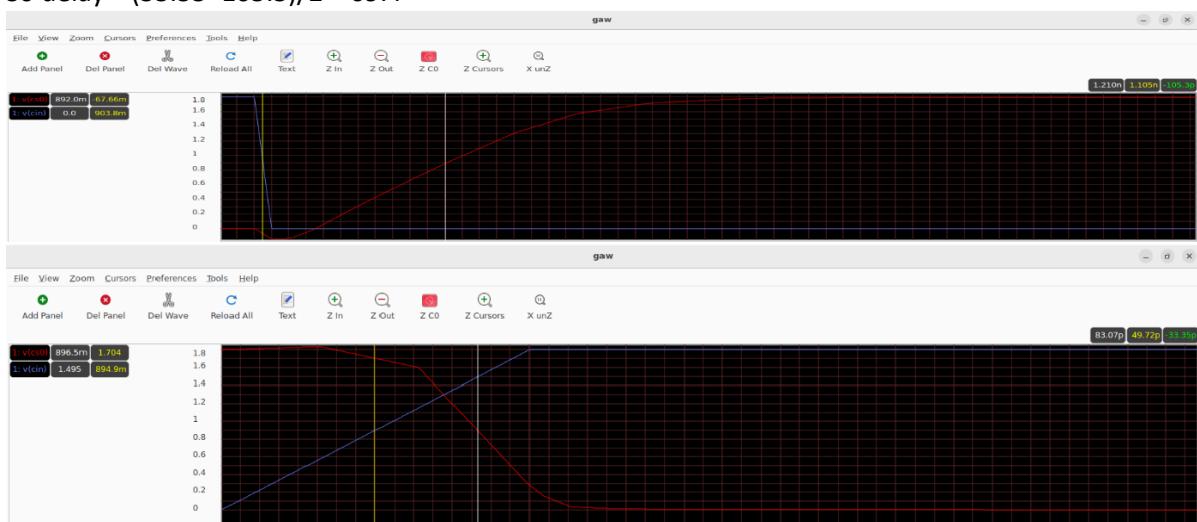
$$S0 \text{ delay} = (33.35+105.3)/2 = 69.4$$



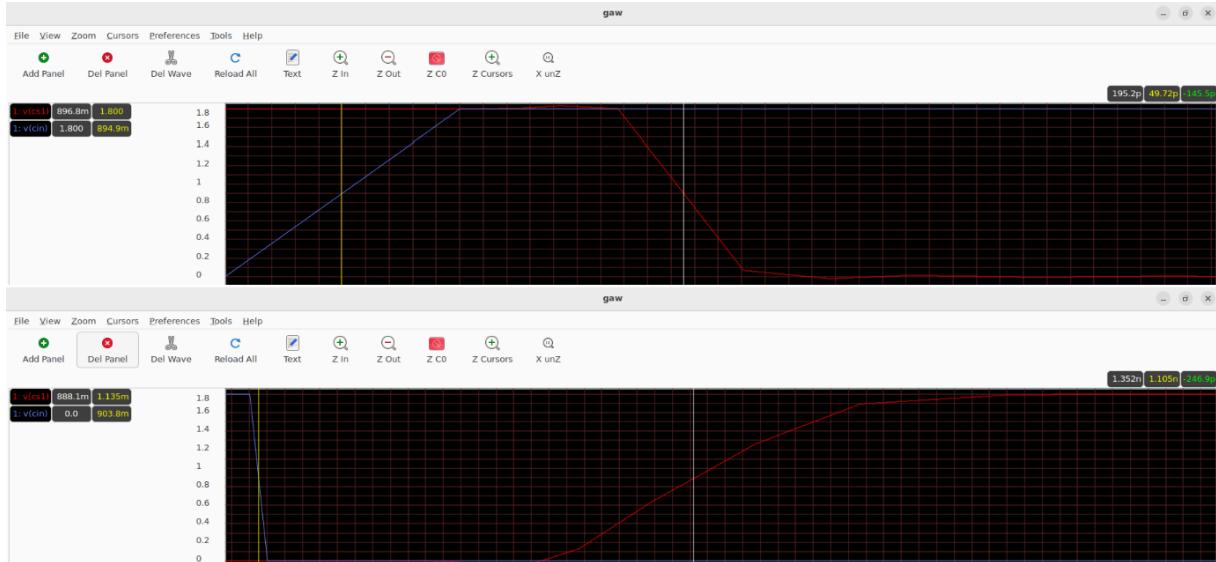
$$S1 \text{ delay} = (145 + 246)/2 = 195.5\text{p}$$


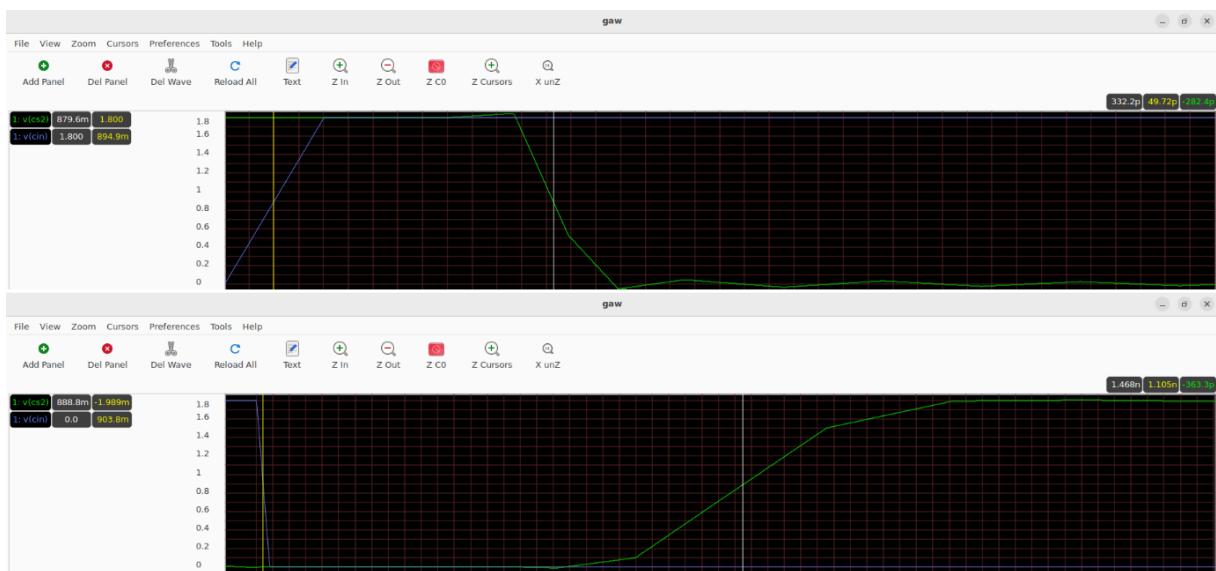
$$S2 \text{ delay} = (282.4 + 363.3)/2 = 322.7$$


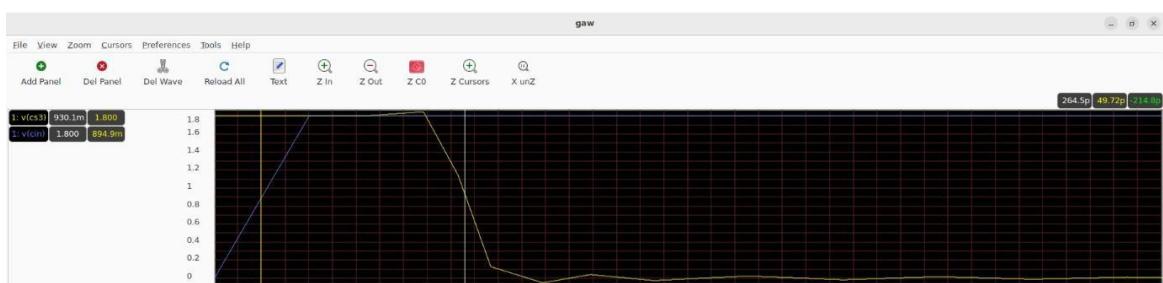
$$S3 \text{ delay} = (214.8 + 239.1)/2 = 226.95\text{p}$$






$$S4 \text{ delay} = (230.5 + 217.9)/2 = 224.2\text{p}$$



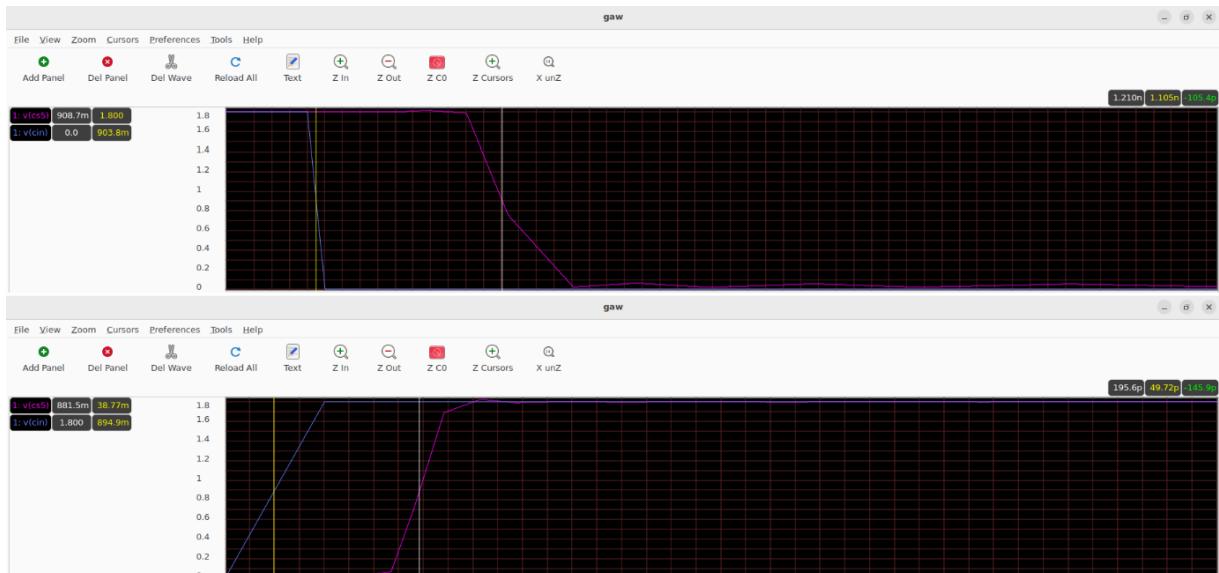
$$S5 \text{ delay} = (105 + 145)/2 = 125\text{p}$$




SF corner Temperature (-40)

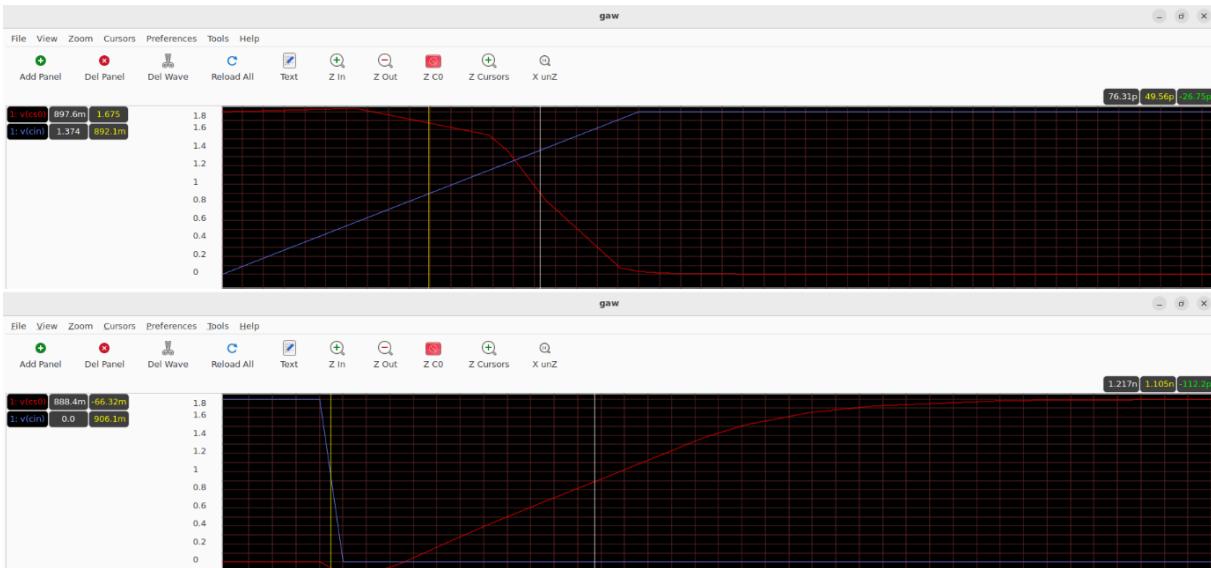
$$S0 \text{ delay} = (26.75 + 112.2)/2 = 69.475\text{p}$$



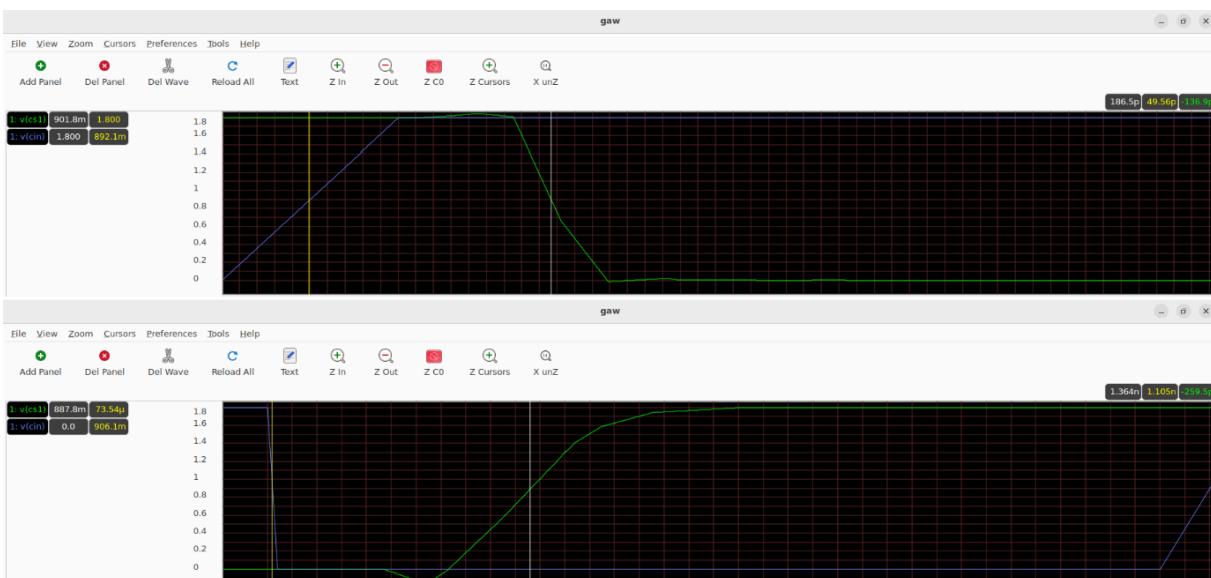
$$S1 \text{ delay} = (136.9 + 259.5)/2 = 198.2\mu\text{s}$$



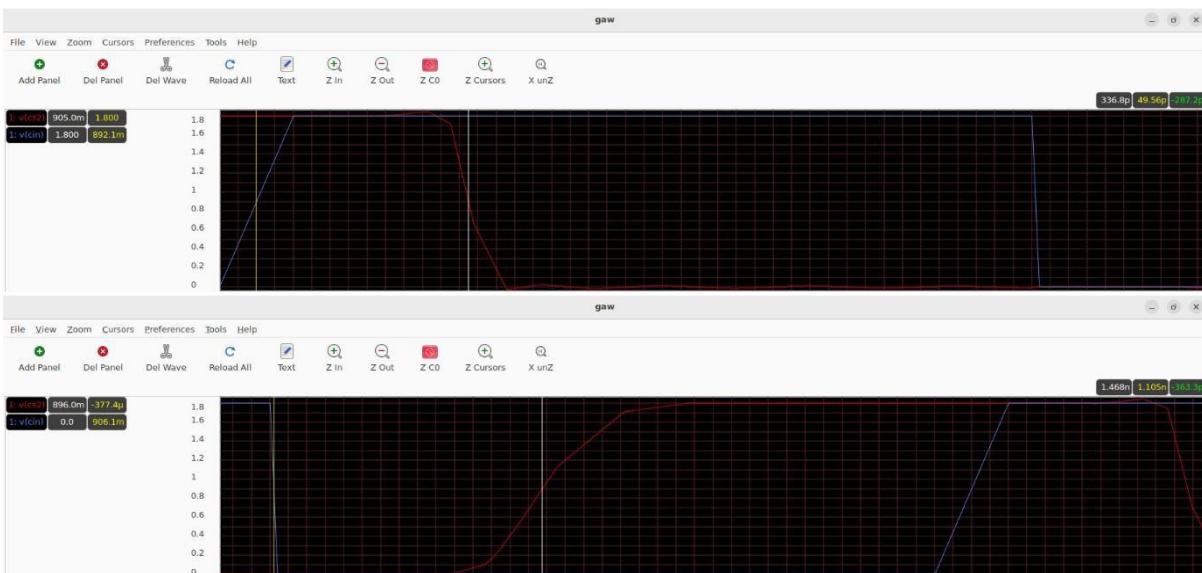
$$S2 \text{ delay} = (287.2 + 363.3)/2 = 325.15$$



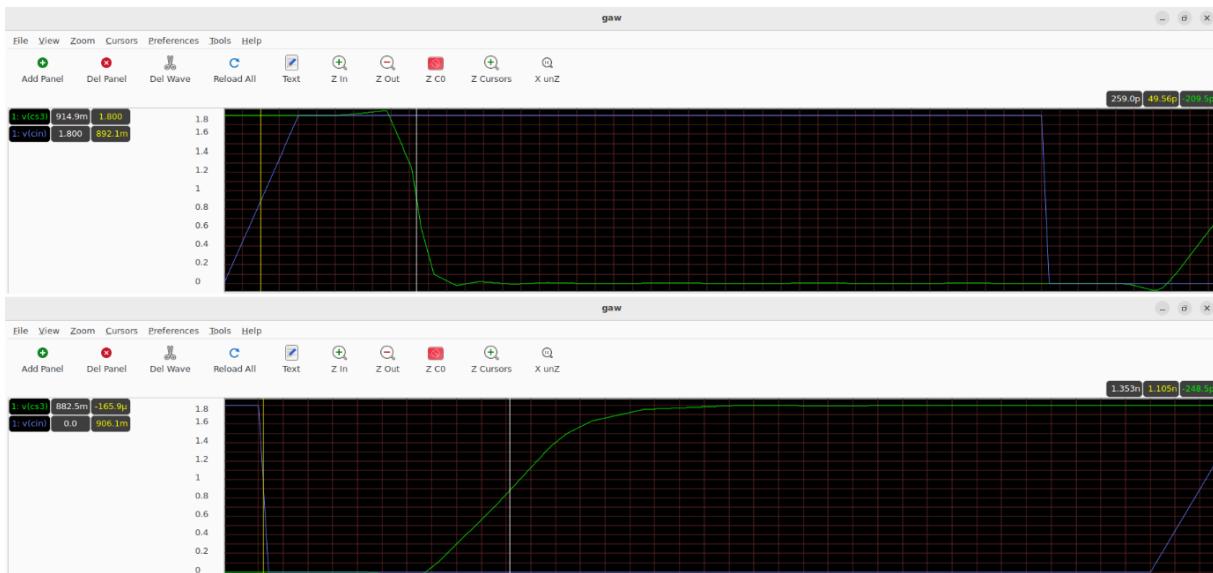
$$S3 \text{ delay} = (209+248.5)/3 = 228.75$$



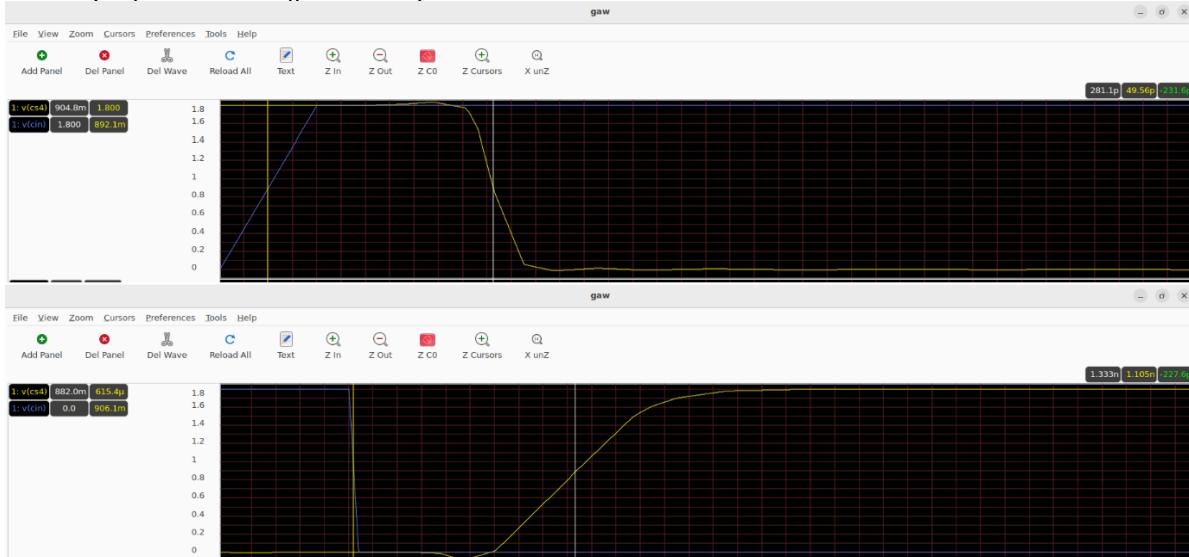
$$S4 \text{ delay} = (231.6+227.6)/2 = 229.6p$$



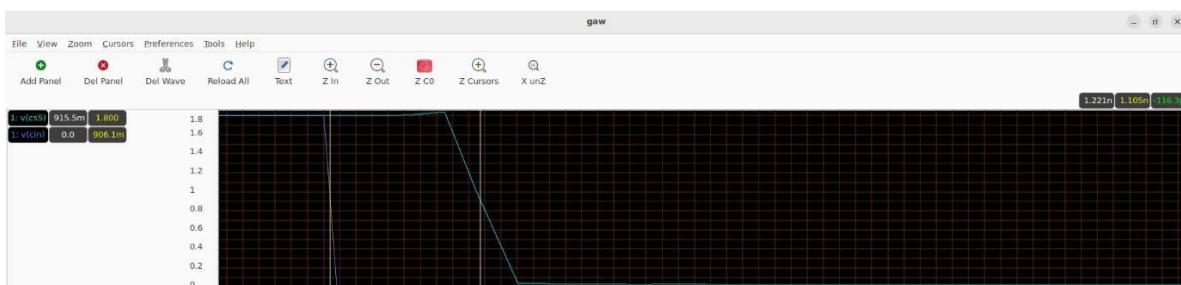
$$S5 \text{ delay} = (116+136)/2 = 126p$$



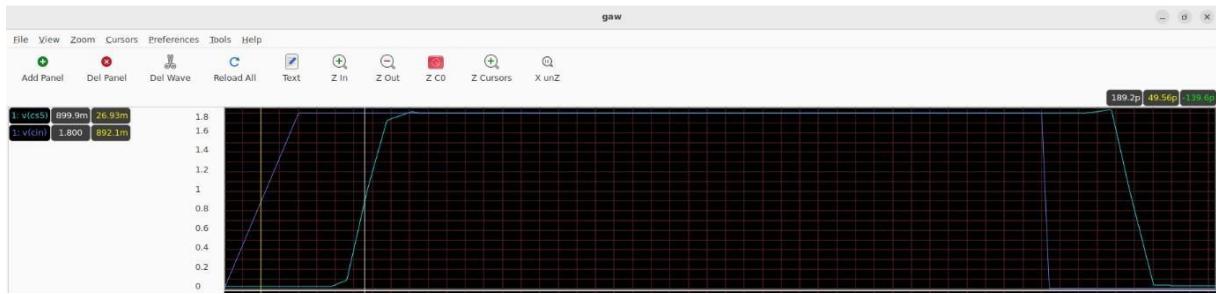


SF corner Temperature (125)

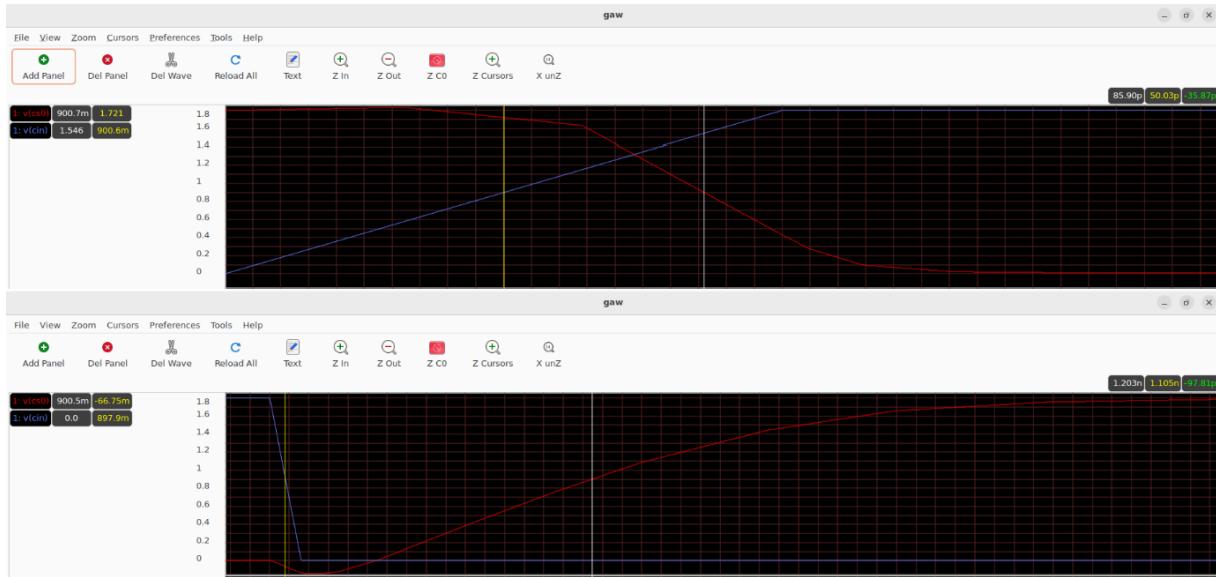
$$S0 \text{ delay} = (35.87 + 97.81)/2 = 66.84\text{p}$$



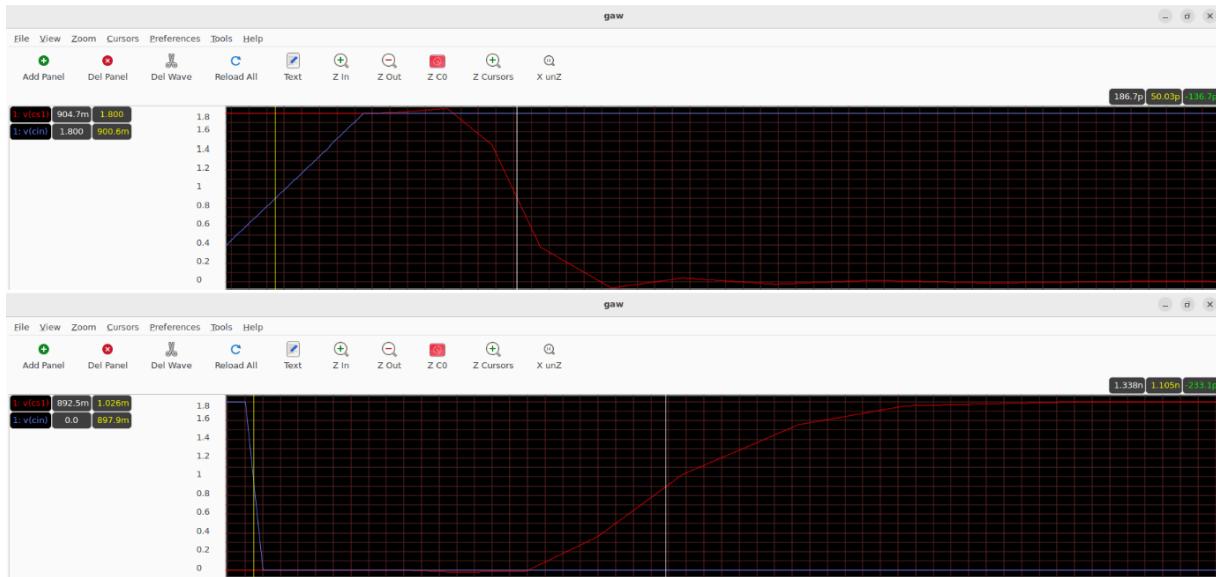
$$S1 \text{ delay} = (136.7 + 233.1)/2 = 184.9\text{p}$$



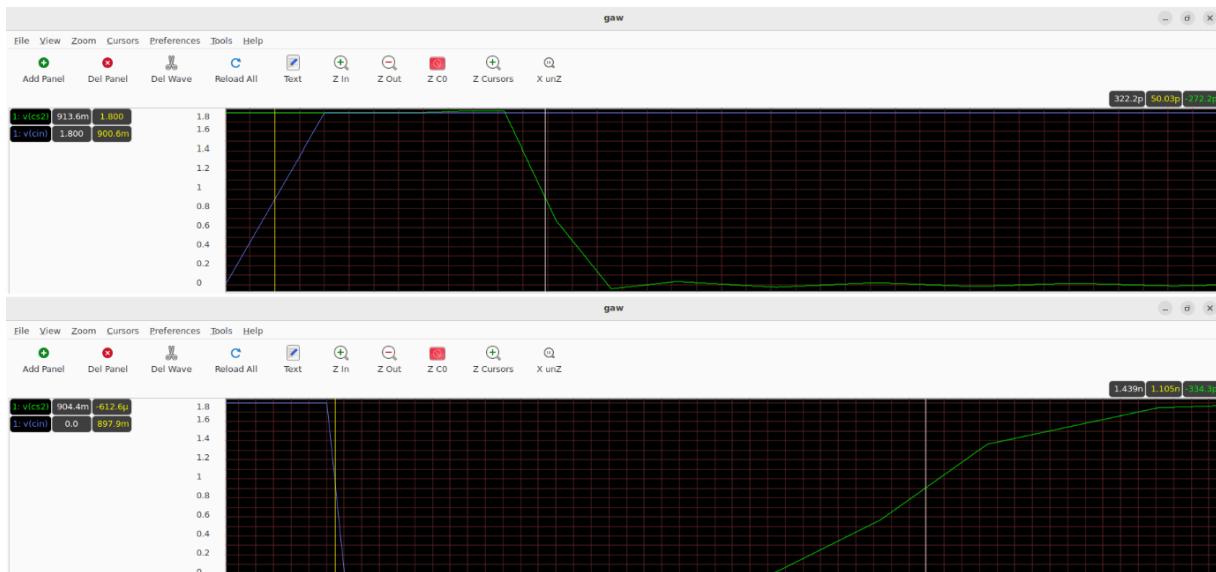
$$S2 \text{ delay} = (272 + 334)/2 = 303\text{p}$$



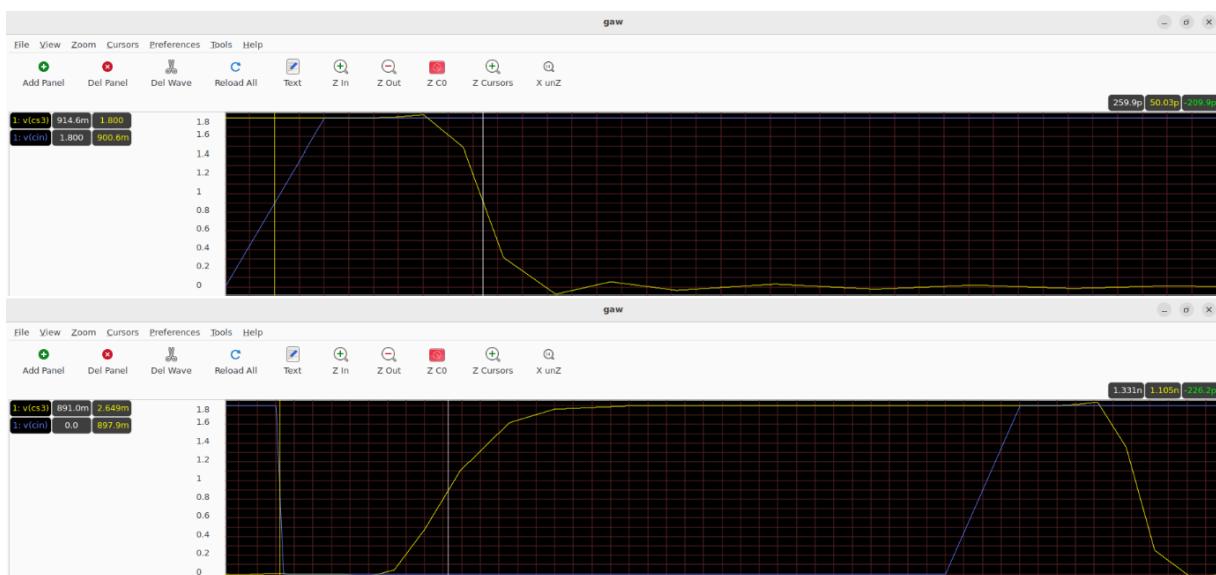
$$S3 \text{ delay} = (209+226)/2 = 217.5\text{p}$$


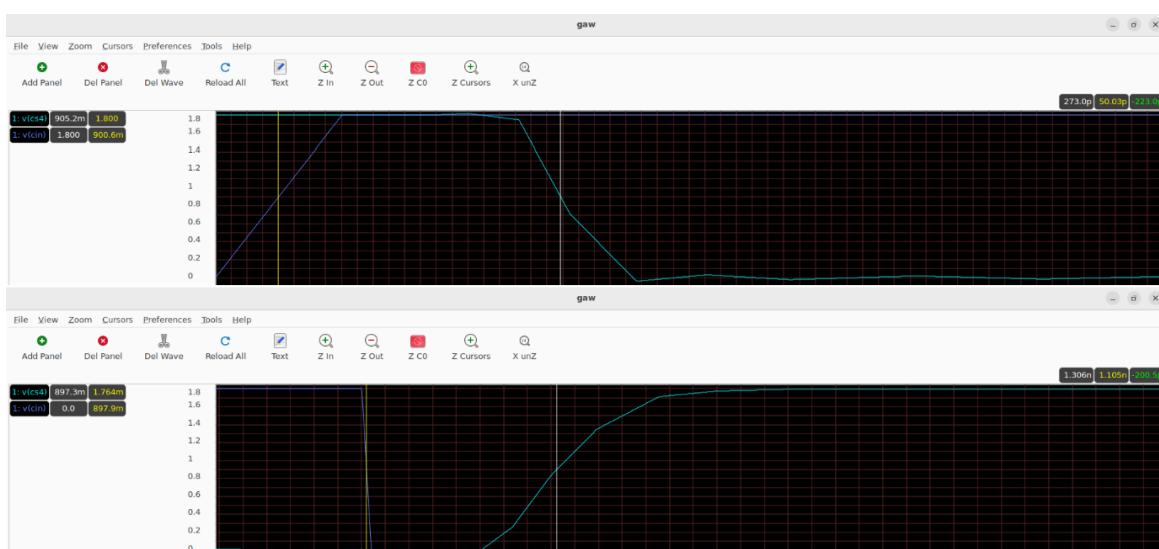
$$S4 \text{ delay} = (223+200)/2 = 211.5\text{p}$$



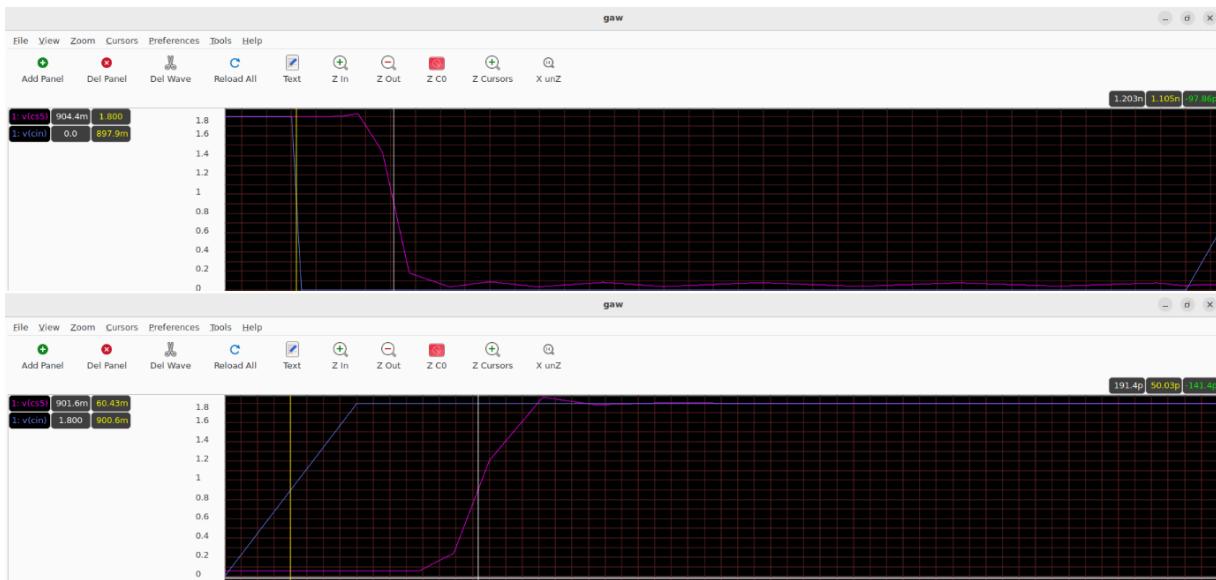
$$S5 \text{ delay} = (97.6 + 141.4)/2 = 119.5\text{p}$$




FF corner – Temperature (-40)

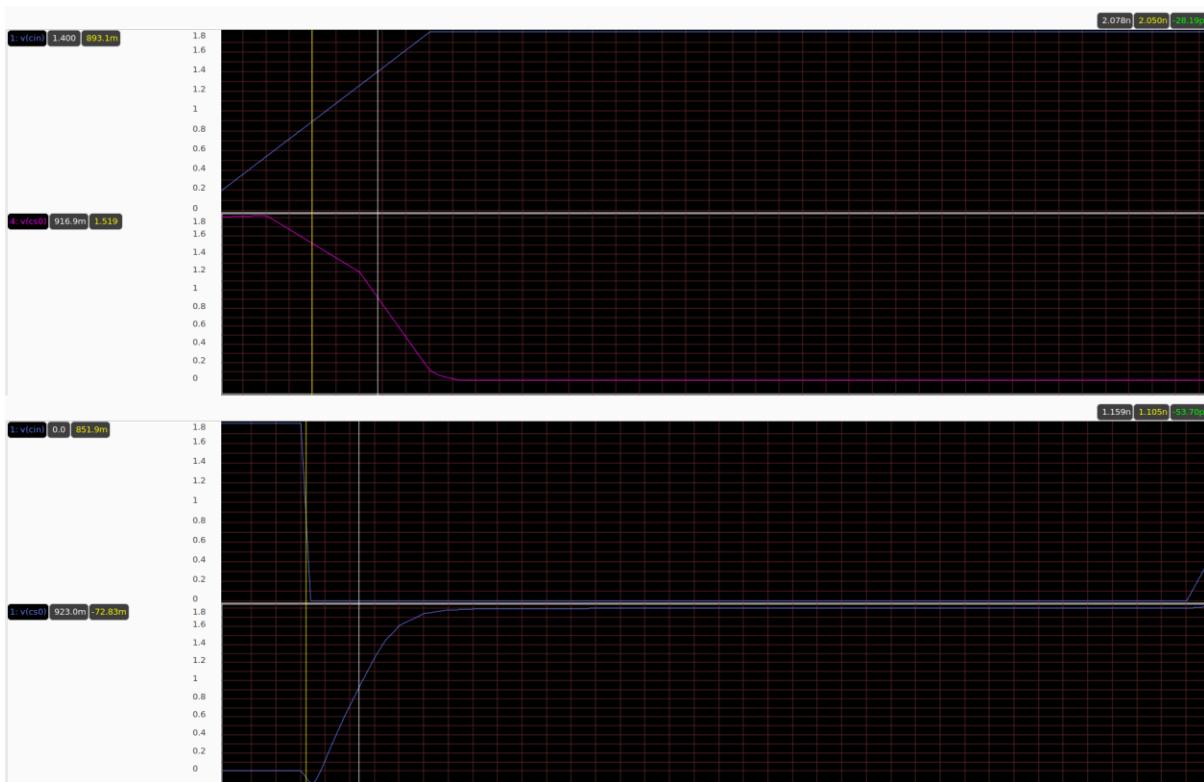
$$S0 \text{ delay} = (28.19 + 53.7)/2 = 40.945\text{p}$$



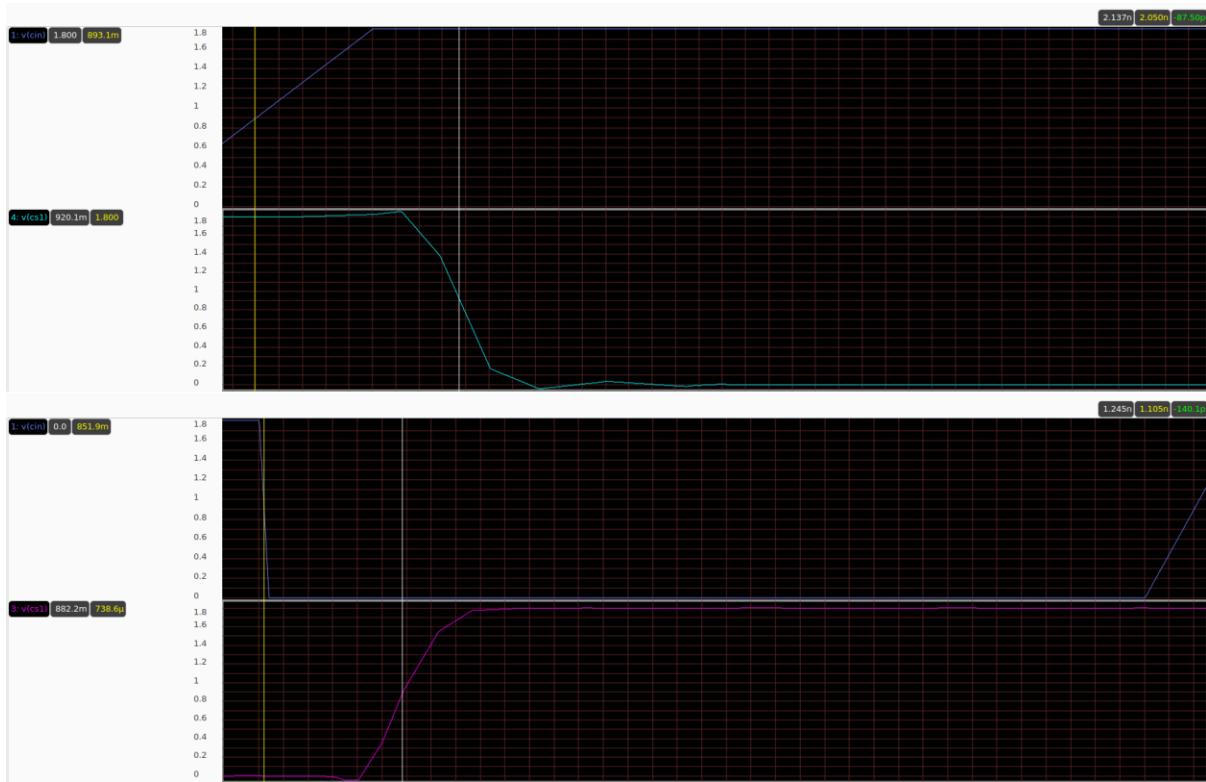
$$S1 \text{ delay} = (87.50 + 140.1)/2 = 113.8\text{p}$$



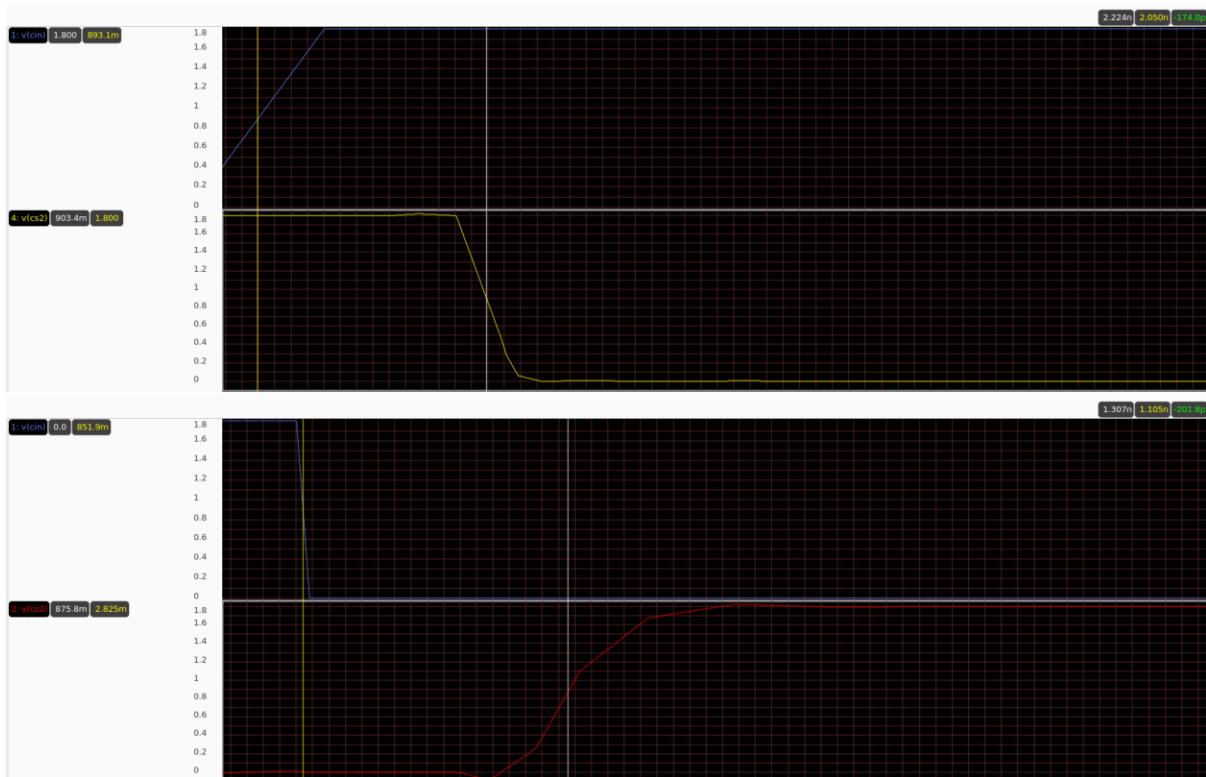
$$S2 \text{ delay} = (174+201)/2 = 187.5\text{p}$$



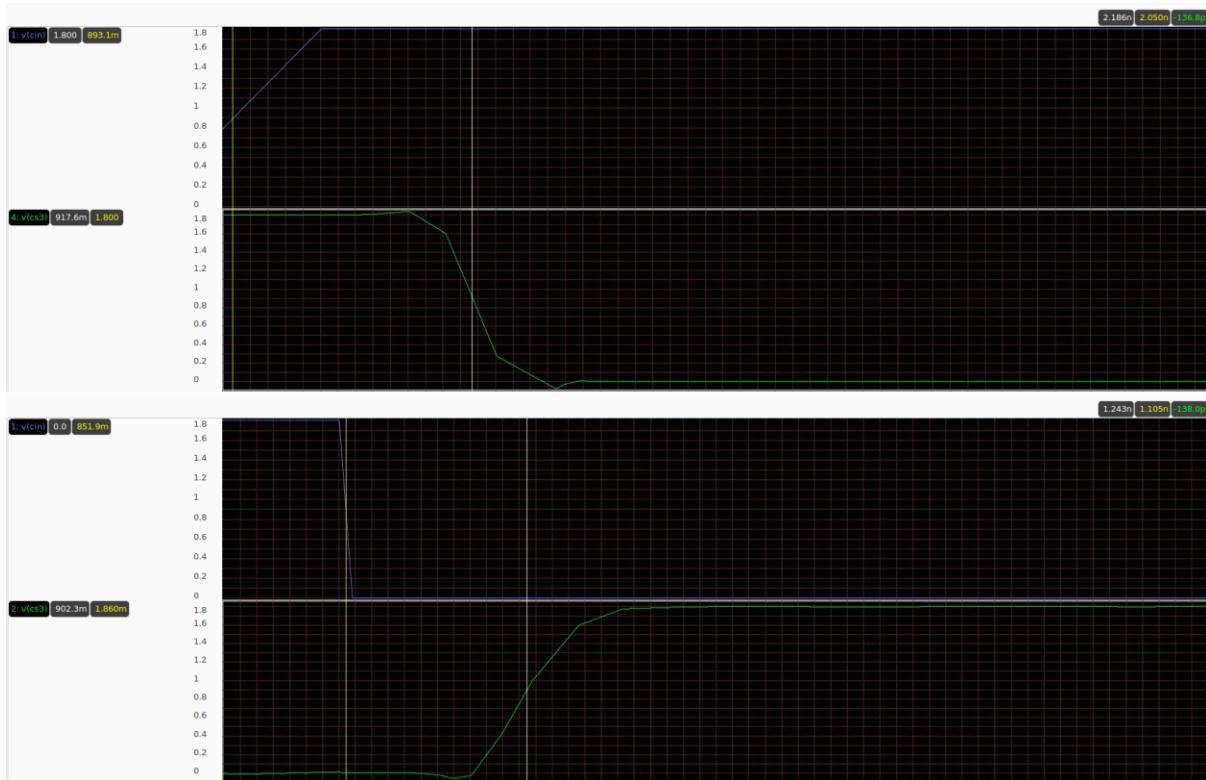
$$S3 \text{ delay} = (136.8+138.0)/2 = 137$$


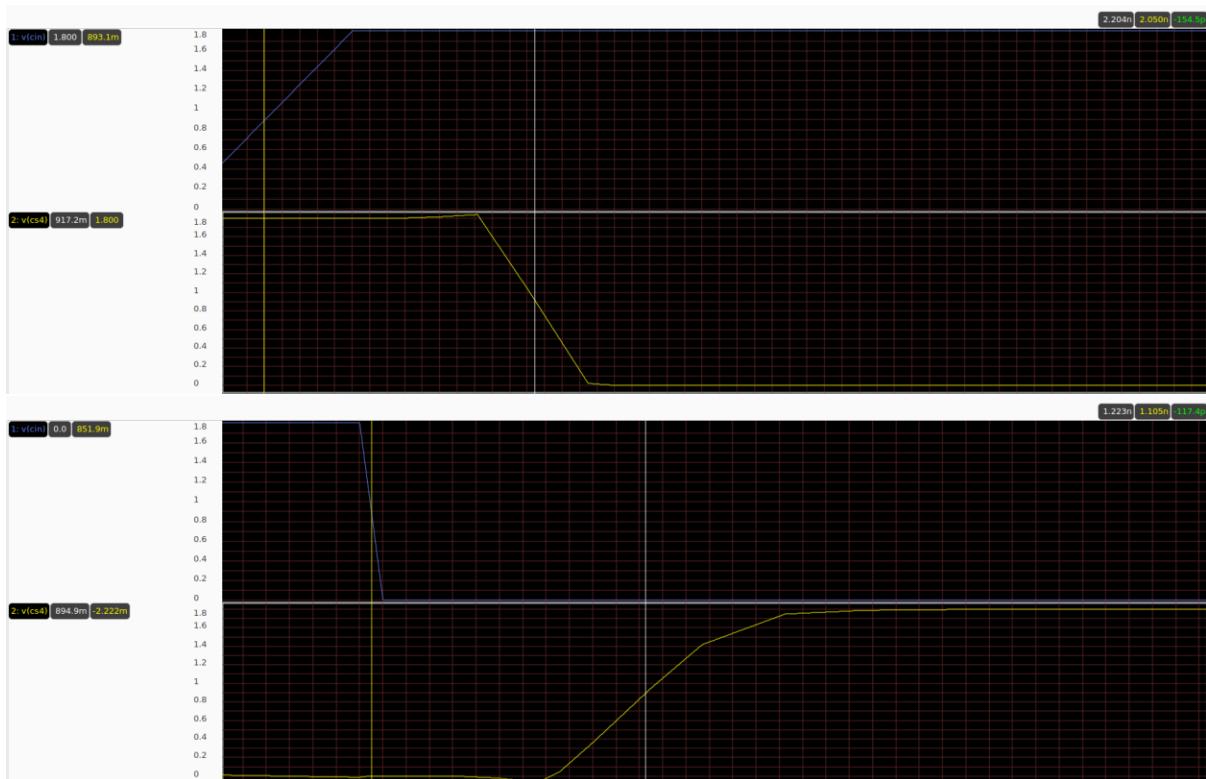
$$S4 \text{ delay} = (154 + 117.4)/2 = 135.7$$



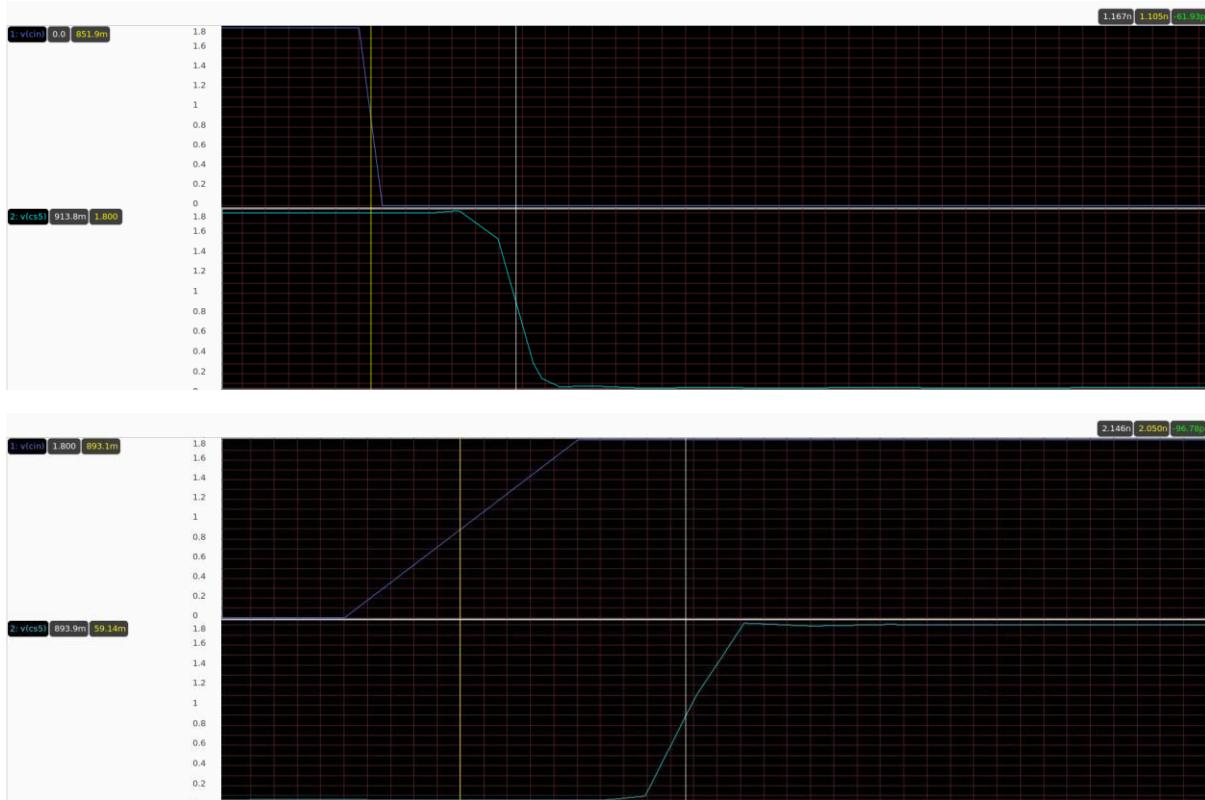
$$S5 \text{ delay} = (61.93 + 96.778)/2 = 79.355\mu$$




FF corner – Temperature (27)
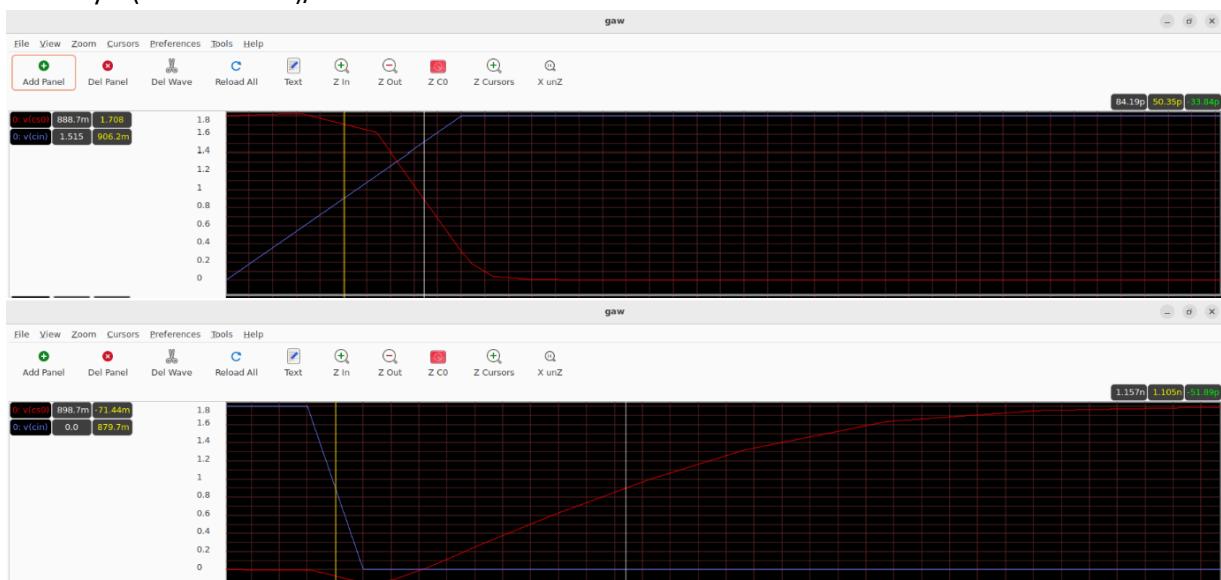
$$SO \text{ delay} = (33.84 + 51.89)/2 = 42.865$$



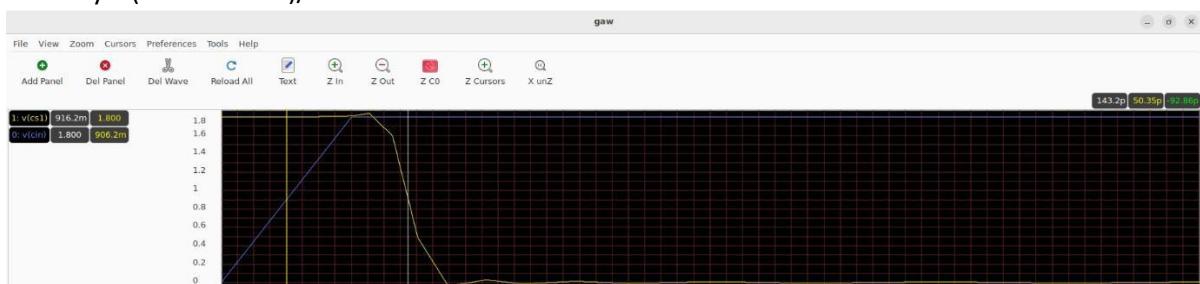
$$S1 \text{ delay} = (92.86 + 142.7)/2 = 117.78$$






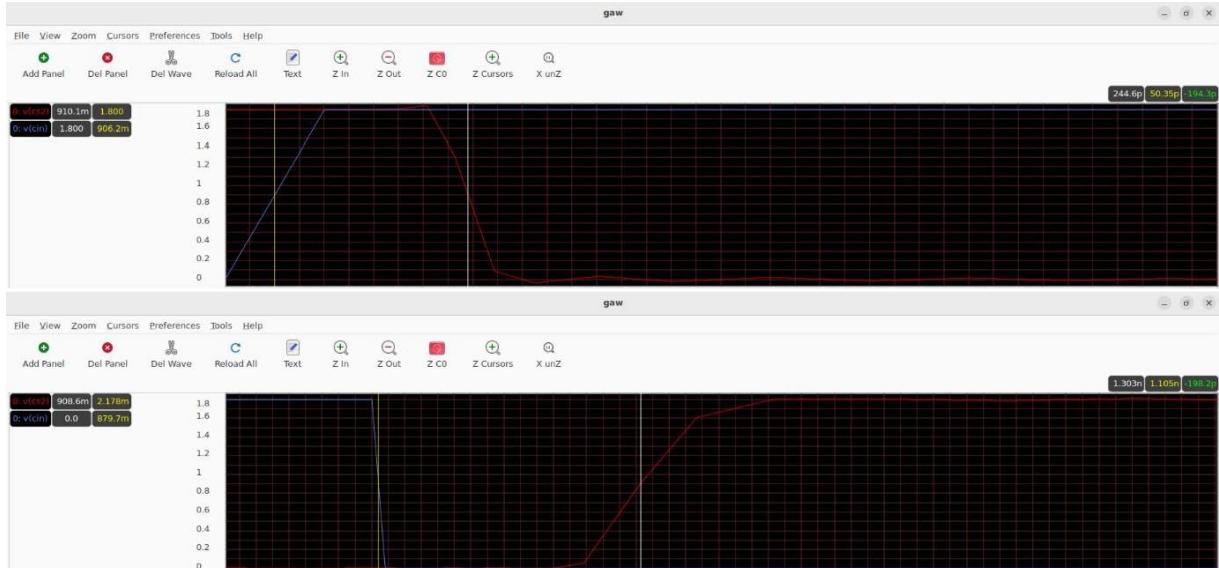
$$S2 \text{ delay} = (194.3 + 198.2)/2 = 196.25$$


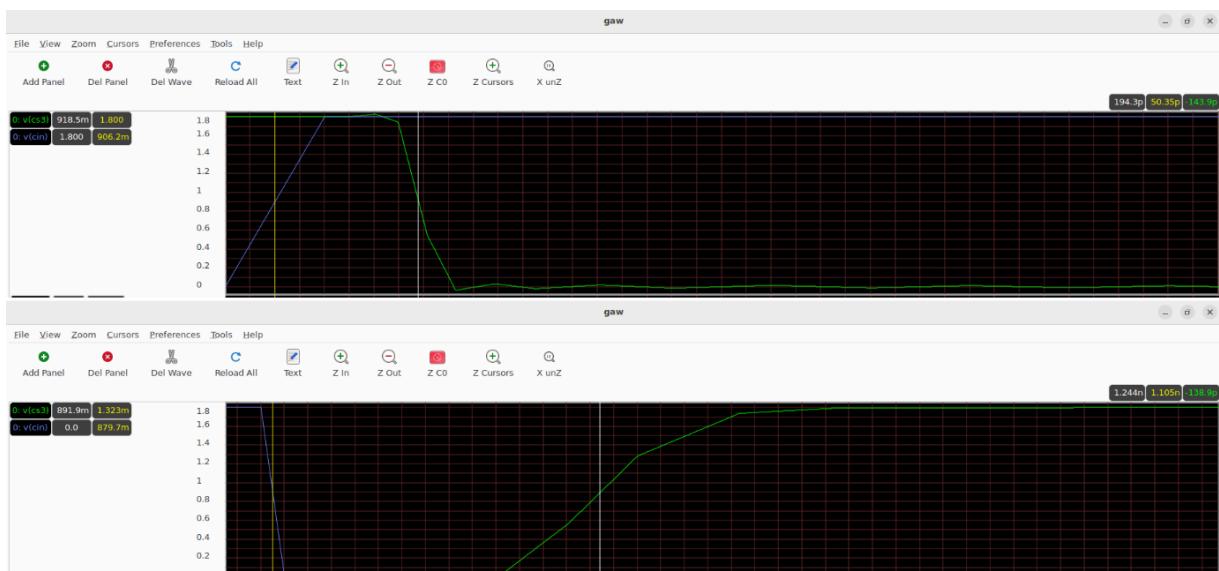
$$S3 \text{ delay} = (141.9 + 138.9)/2 = 140.4$$


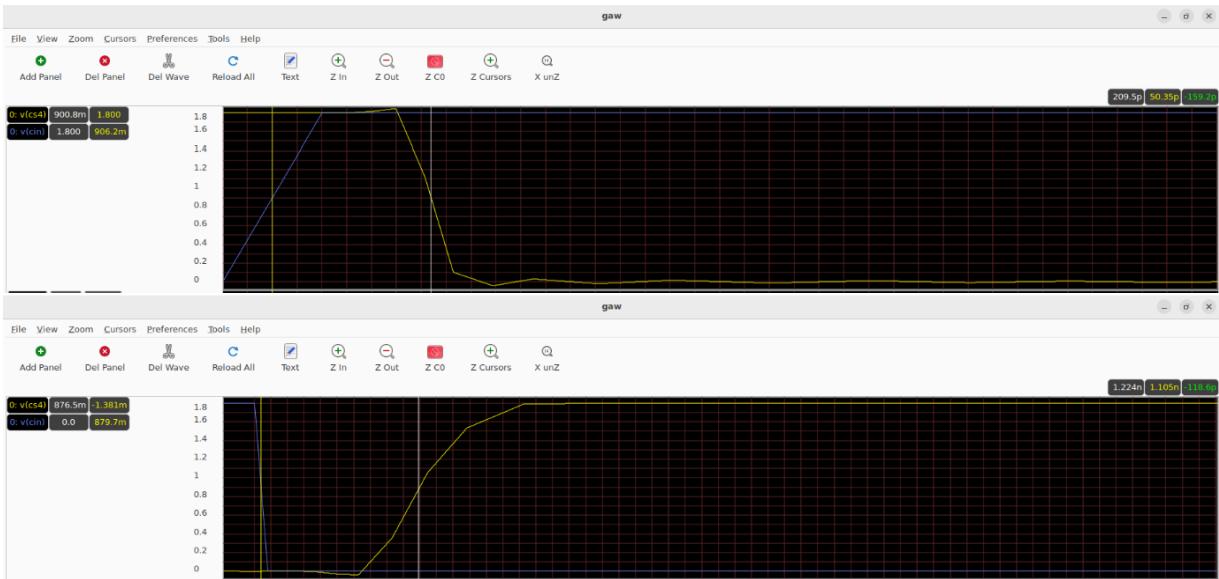
$$S4 \text{ delay} = (159.2 + 118.6)/2 = 138.9$$





$$S5 \text{ delay} = (63.28 + 100.8)/2 = 82.04\text{p}$$




FF corner – Temperature (125)
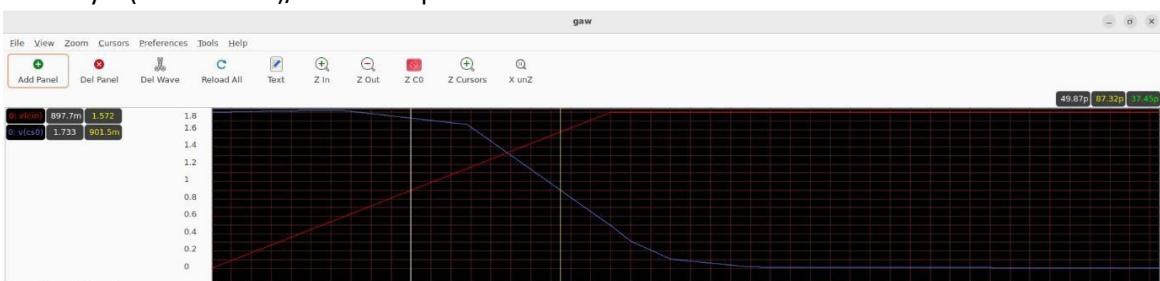
$$S0 \text{ delay} = (37.45 + 50.9)/2 = 44.175\text{p}$$




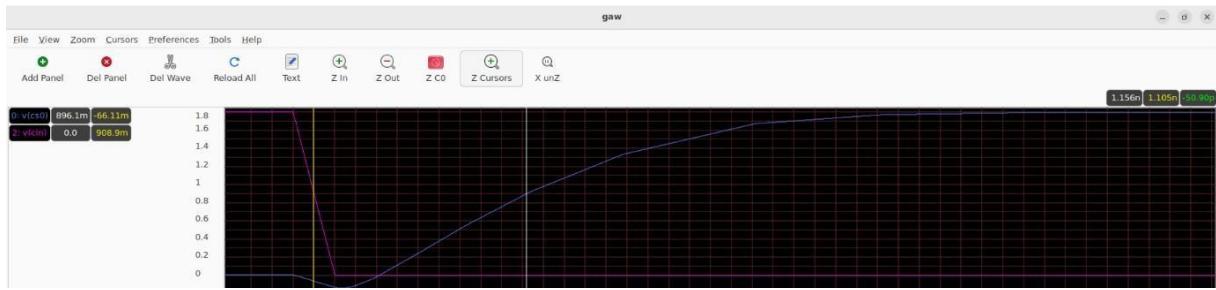

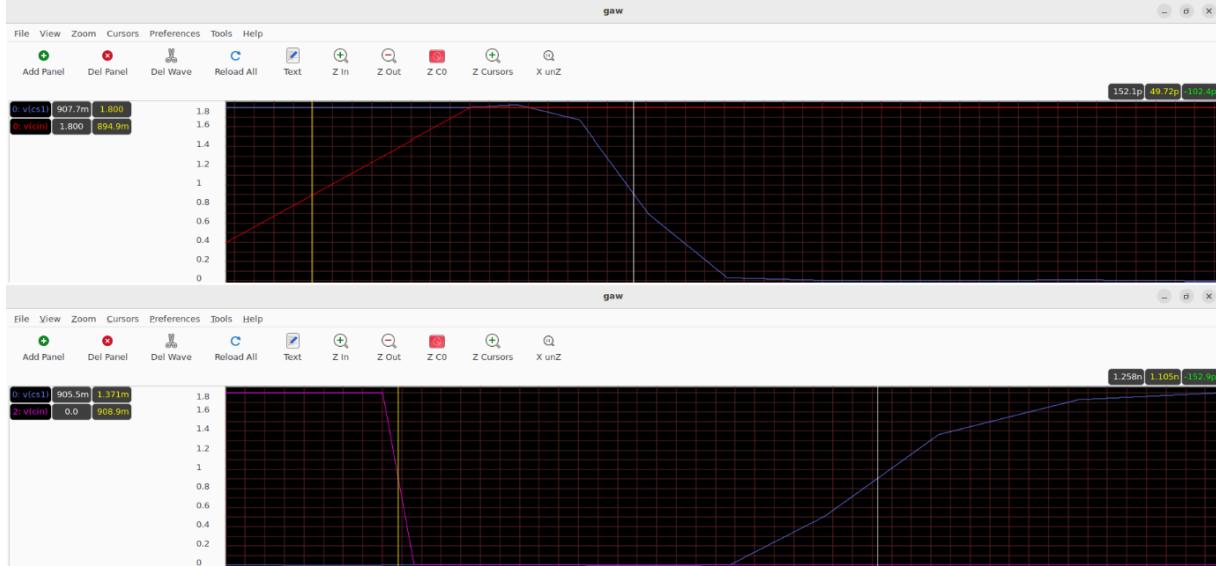
$$S1 \text{ delay} = (102.4 + 152.9)/2 = 127.65\text{p}$$



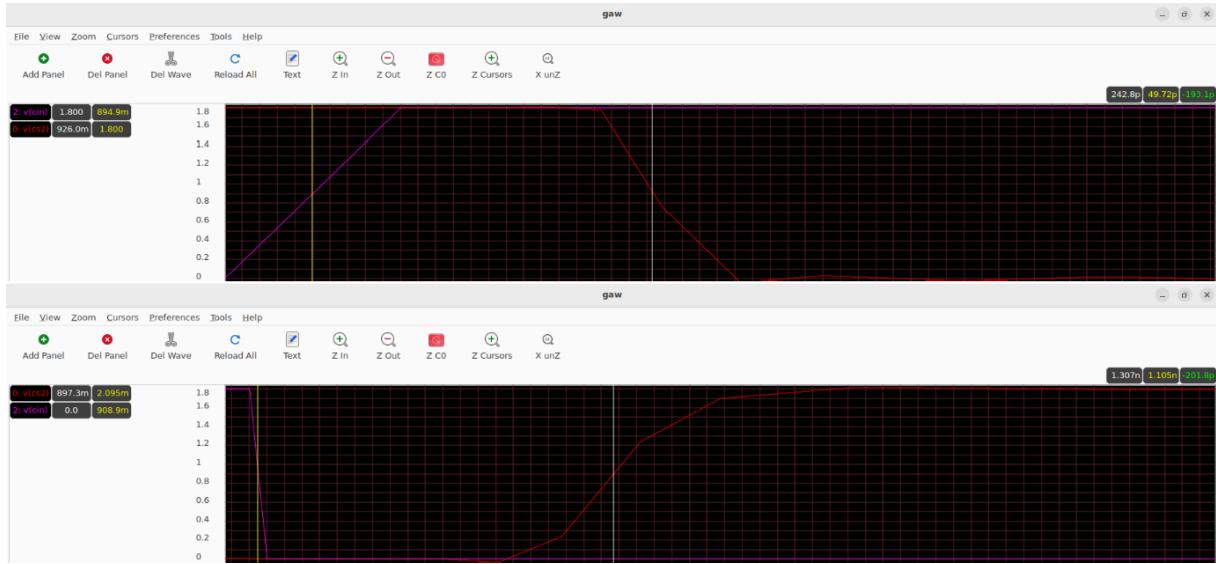
$$S2 \text{ delay} = (193.1+201.8)/2 = 197.45$$


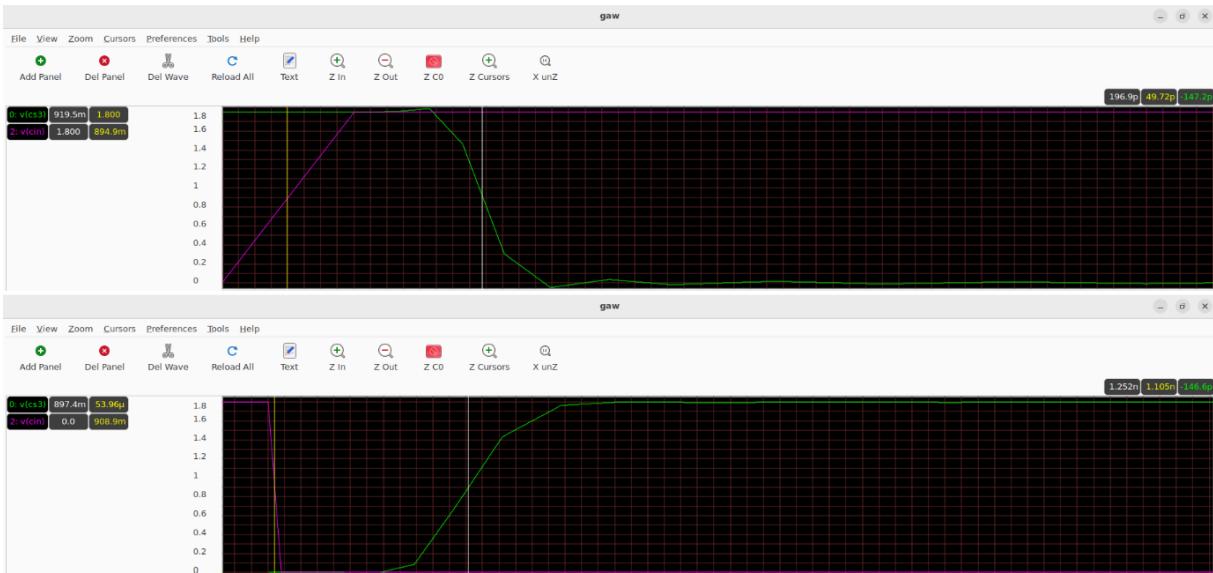
$$S3 \text{ delay} = (147.2+146.6)/2 = 147.4$$


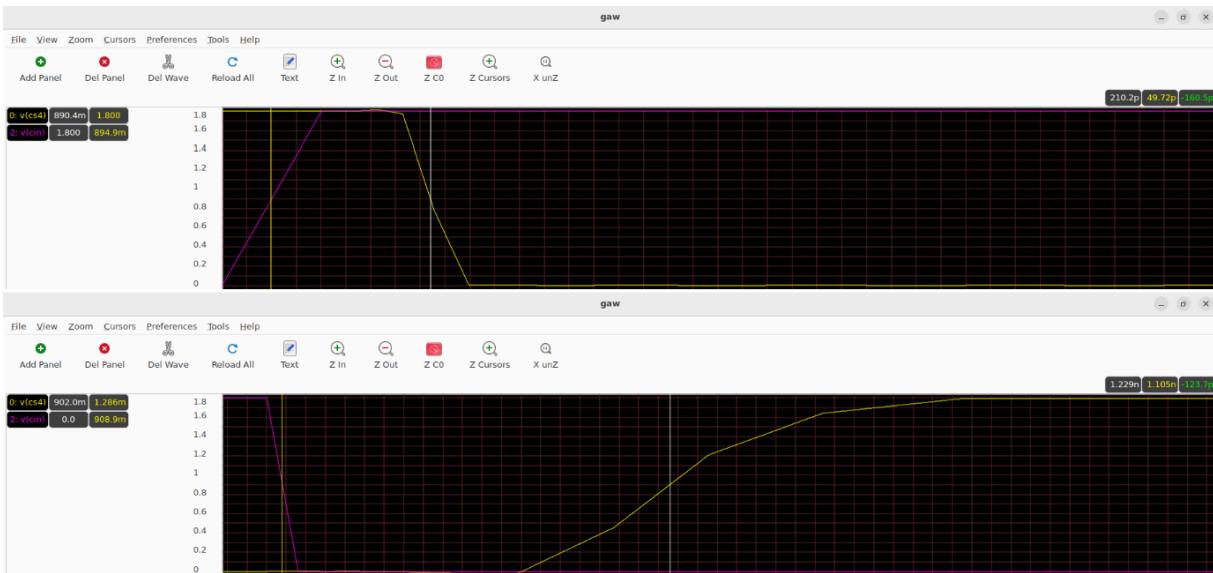
$$S4 \text{ delay} = (160.5 + 123.7)/2 = 142.1\text{p}$$



$$S5 \text{ delay} = (65.19 + 102.1)/2 = 83.645\text{p}$$




TT	-40	27	125
	Delay(ps)	Delay	Delay
S0	56	56	59.5
S1	160	162	166
S2	271	268	270
S3	192	190	192
S4	182	184.5	184.5
S5	107	109	109

SS	-40	27	125
	Delay(ps)	Delay(ps)	Delay(ps)
S0	87	87.5	83.5
S1	247	240	297
S2	388	396.5	389.5
S3	285	276.5	268
S4	277	272.5	269
S5	164	161	153

SF	-40	27	125
	Delay(ps)	Delay(ps)	Delay(ps)
S0	69.475	69.4	66.84
S1	198.28	195.5	184.9
S2	325.15	322.7	303
S3	228.75	226.95	217.5
S4	229.6	224.2	211.5
S5	126	125	119.5

FS	-40	27	125
	Delay(ps)	Delay(ps)	Delay(ps)
S0	56.5	56.34	60.5
S1	154	155.3	173
S2	252	253.95	254.58
S3	181	182.58	191
S4	170.5	170.5	179.5
S5	106.5	106.825	109.58

FF MODEL	-40	27	125
	Delay(ps)	Delay(ps)	Delay(ps)
S0	40.945	42.8686	44.17
S1	113.85	117.70	127.65
S2	187.5	196.25	197.45
S3	137	140.4	147.4
S4	135.7	138.9	142.1
S5	79.35	82.4	83.64

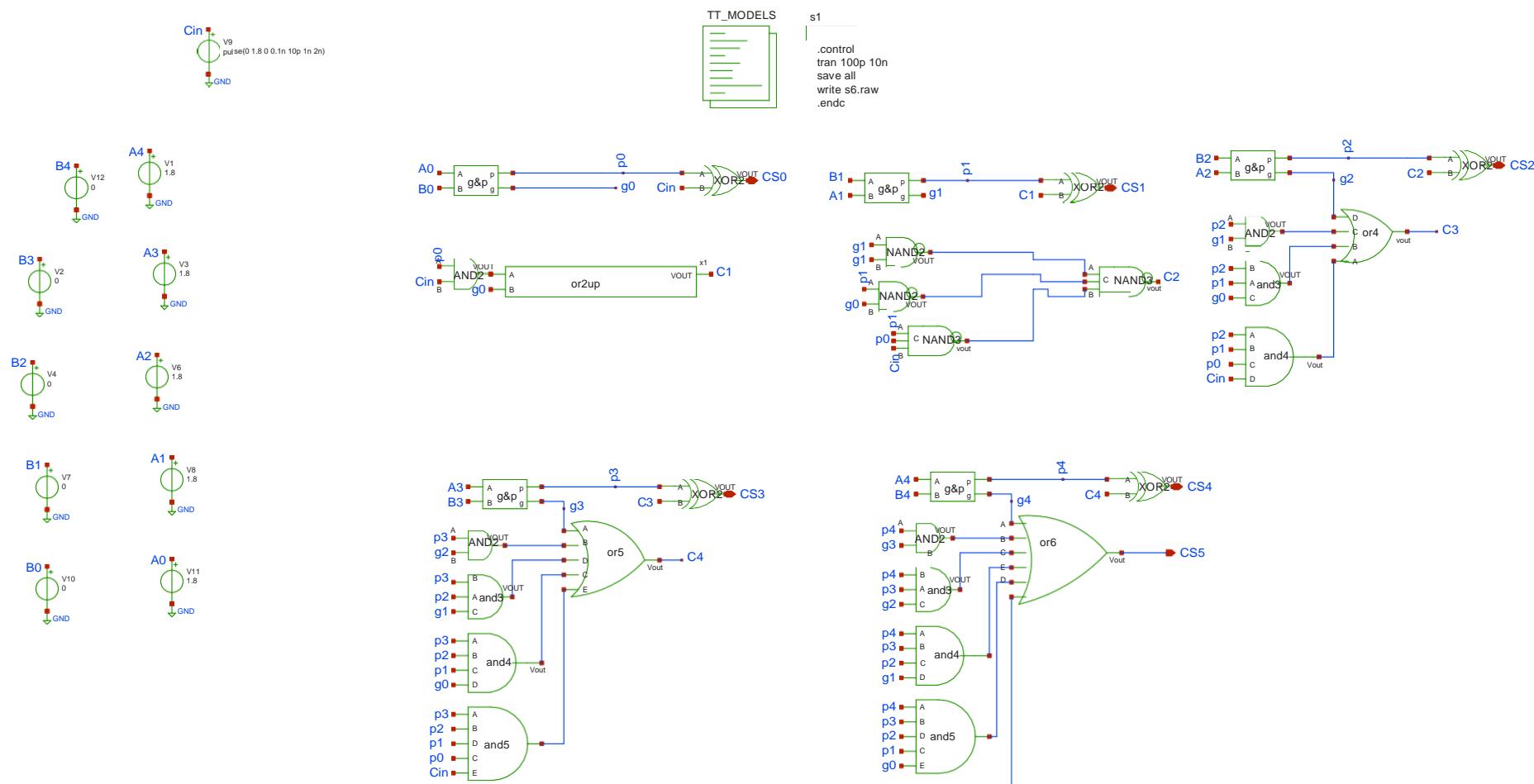


F

Vout


Vout


p1 D and6
p0 E
Cin F

xor2.sch

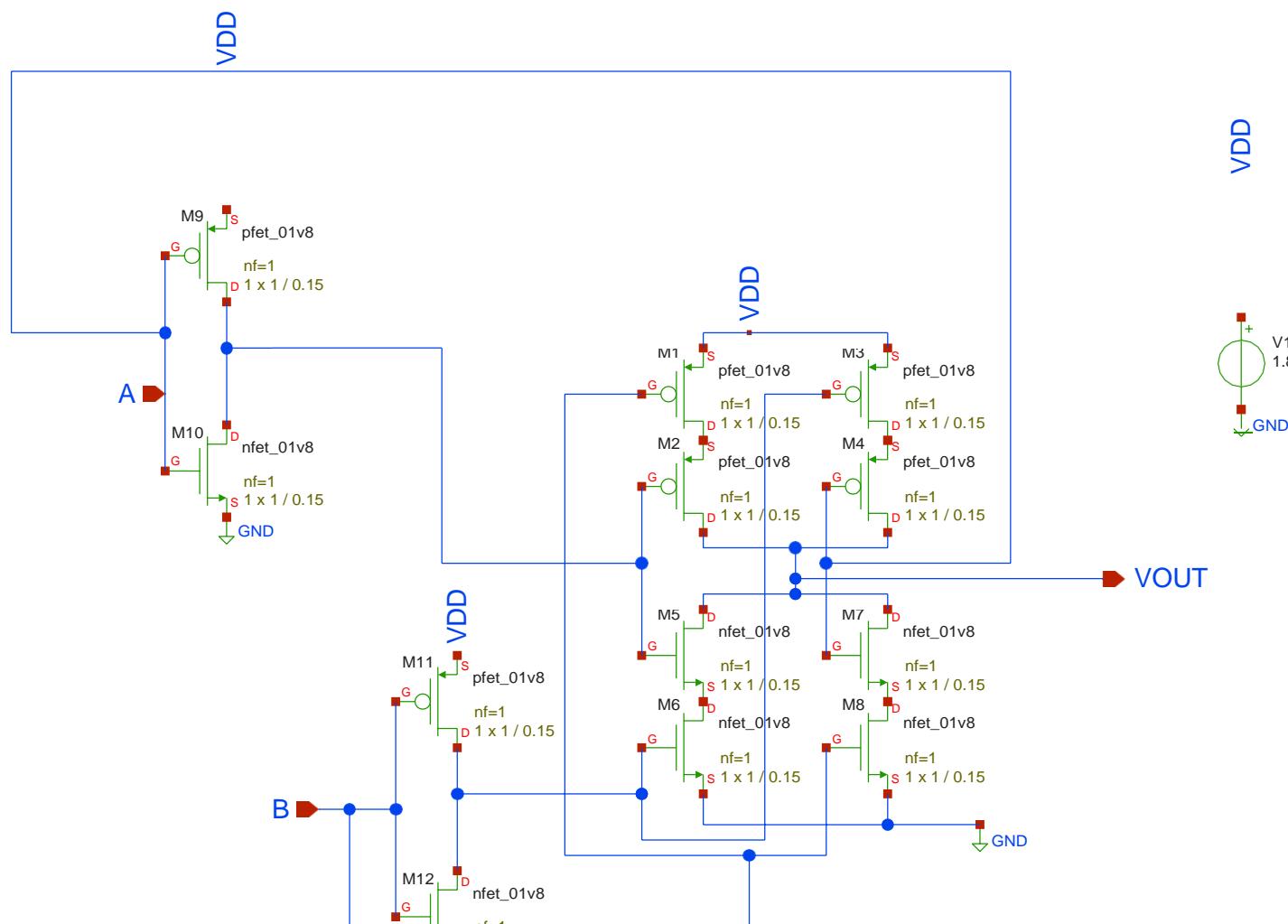

VDD
V1 1.8
GND

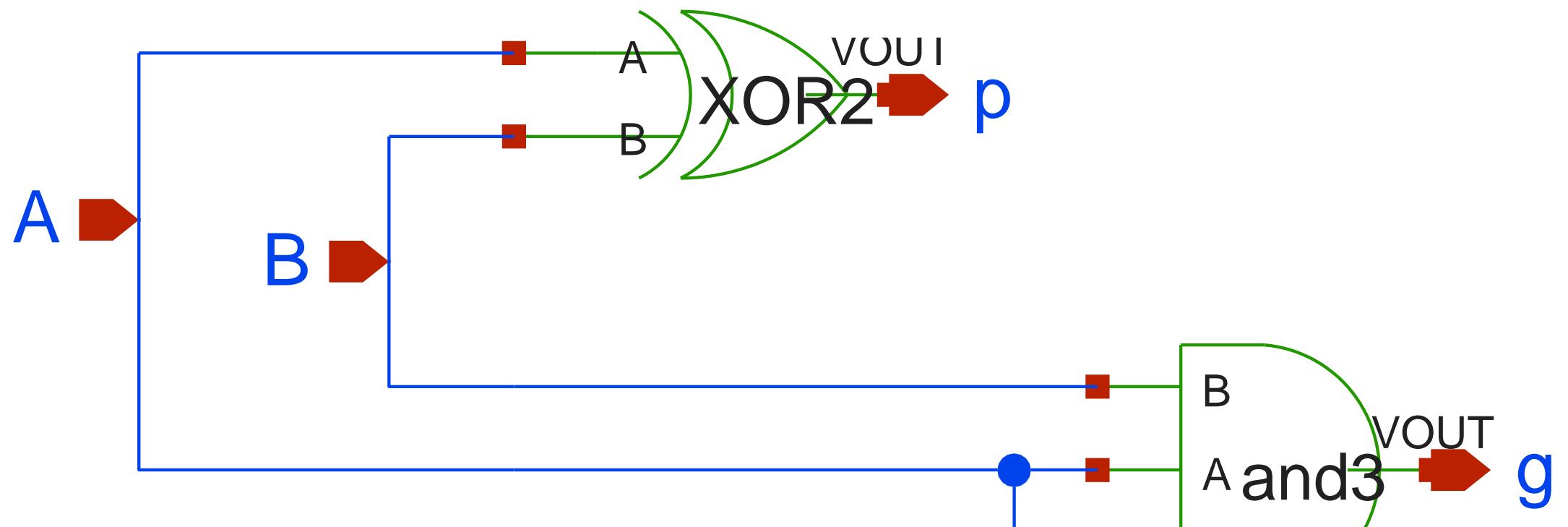

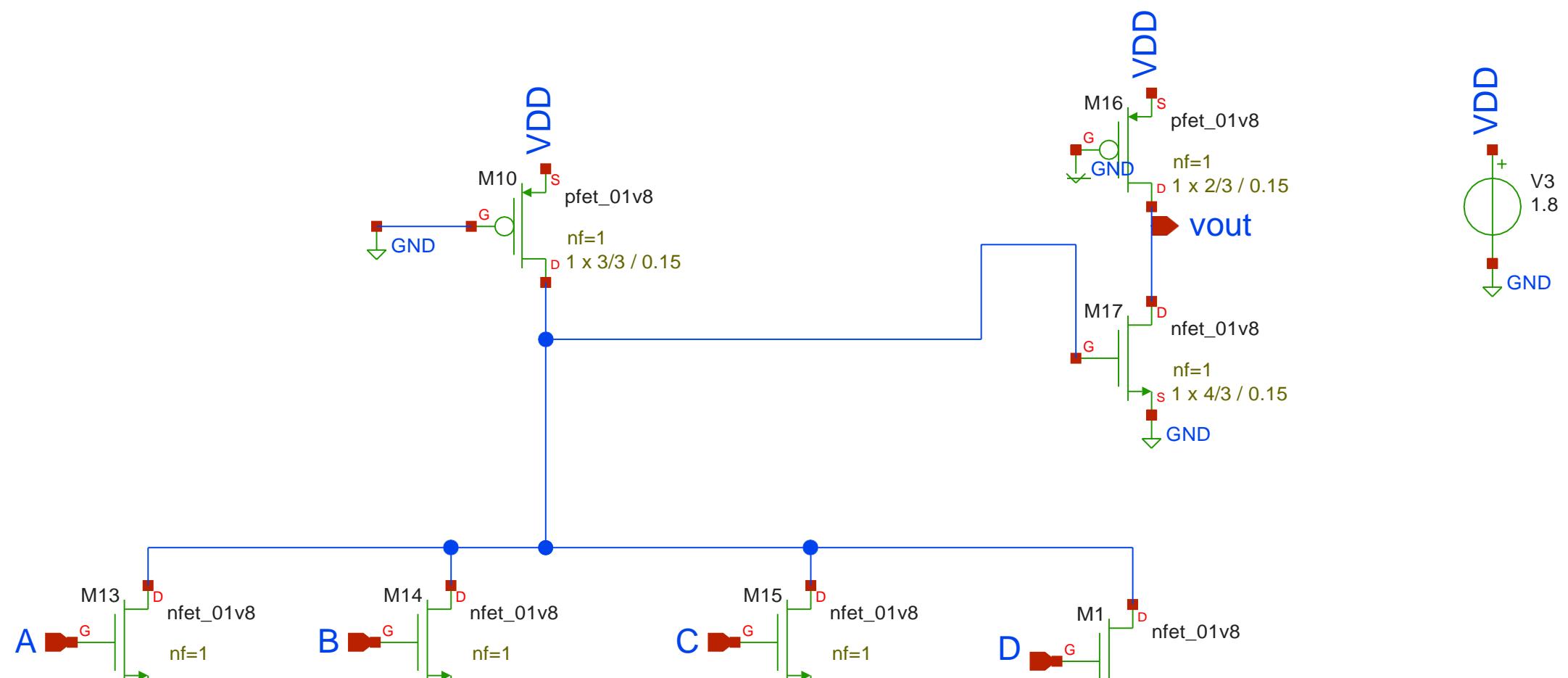

s 1 x 4/3 / 0.15

GND

s 1 x 4/3 / 0.15


 GND

s 1 x 4/3 / 0.15


 GND

nf=1
s 1 x 4/3 / 0.15

GND

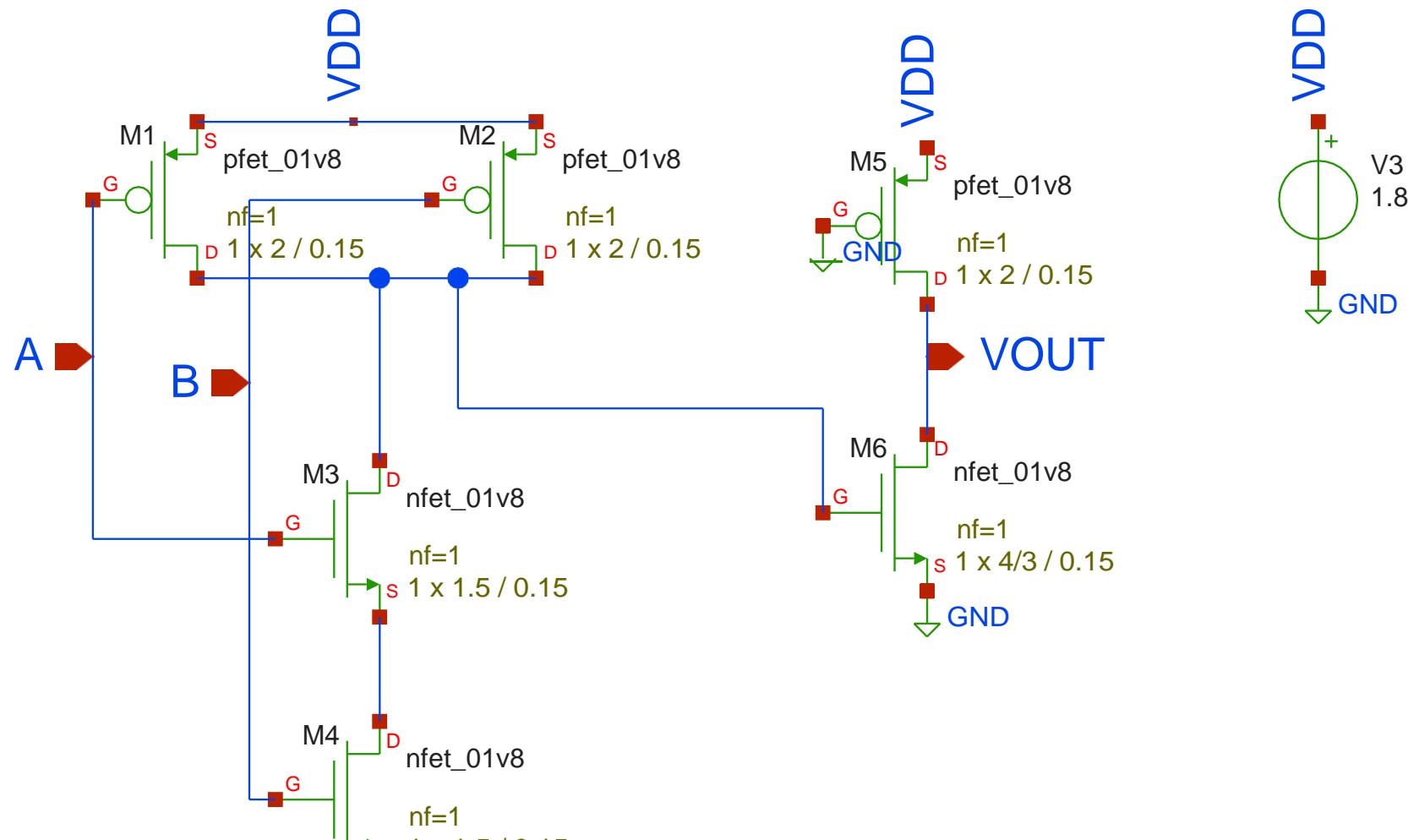


and3.sch

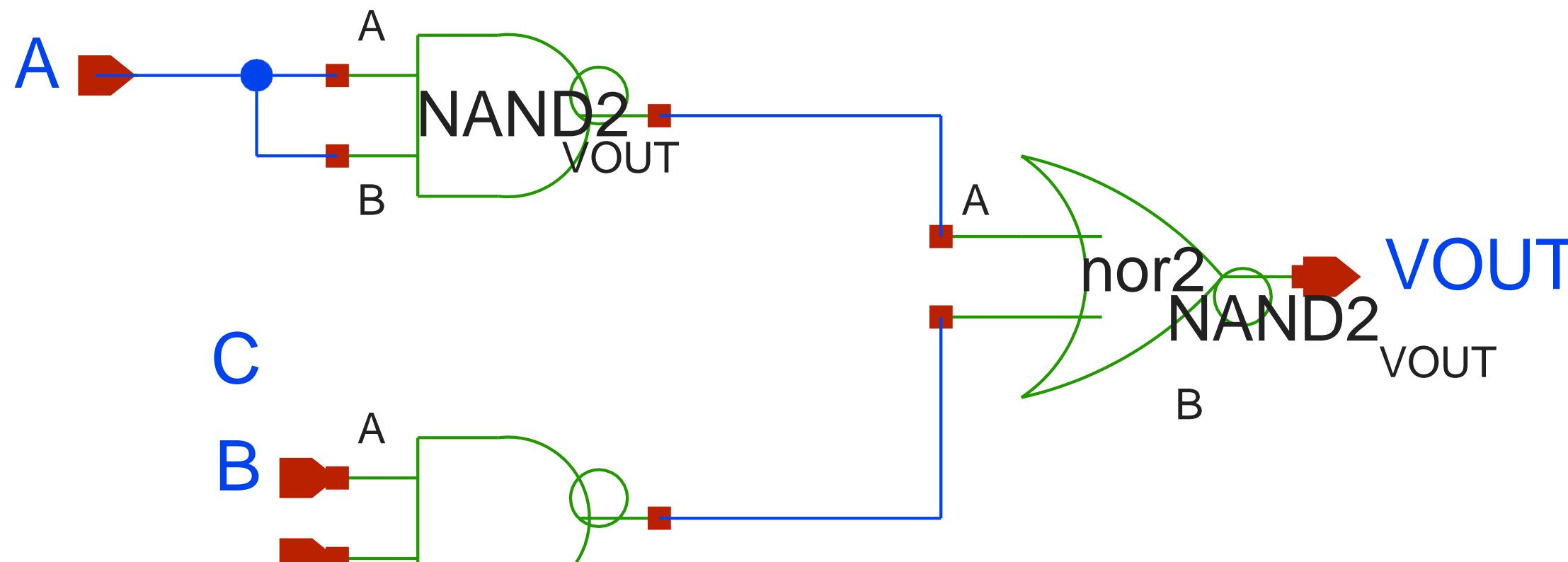


VOUT
B

and4.sch

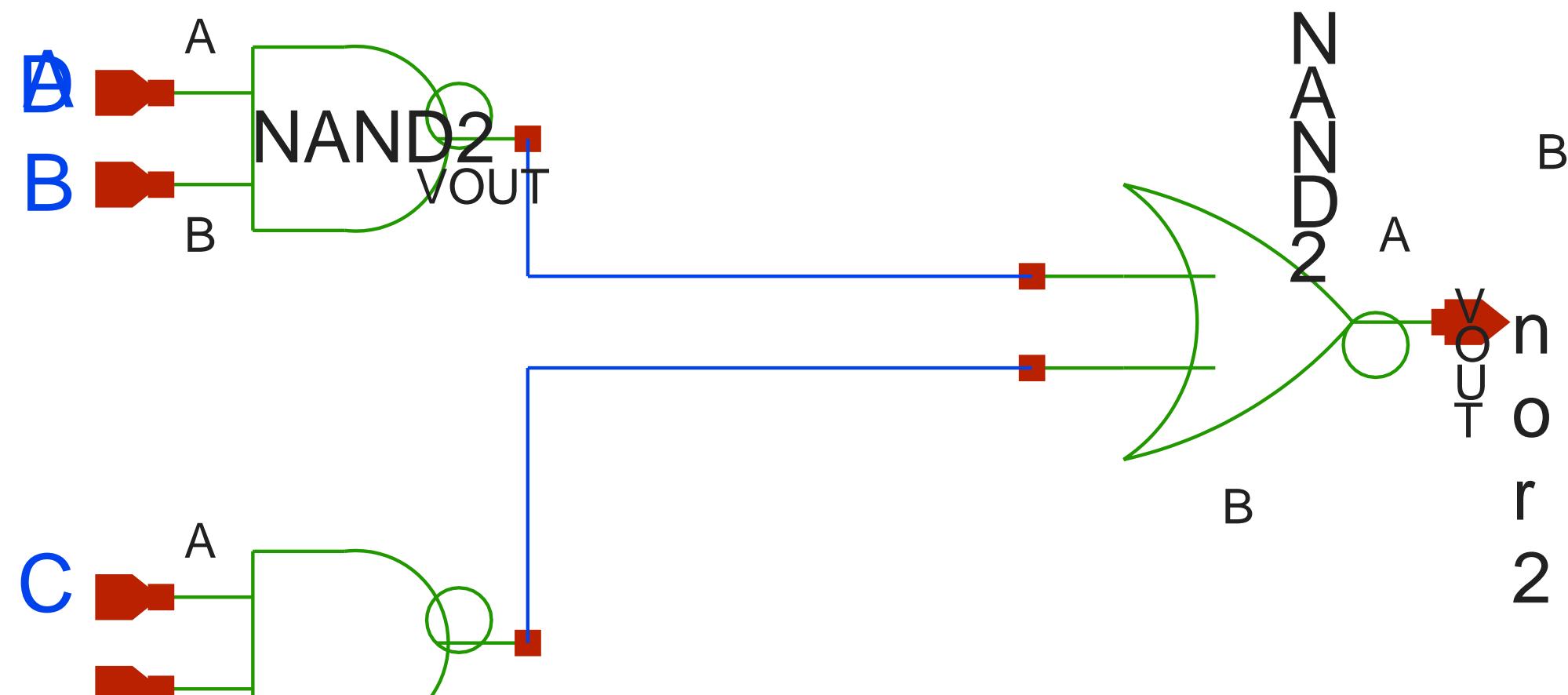

VOUT

Vout

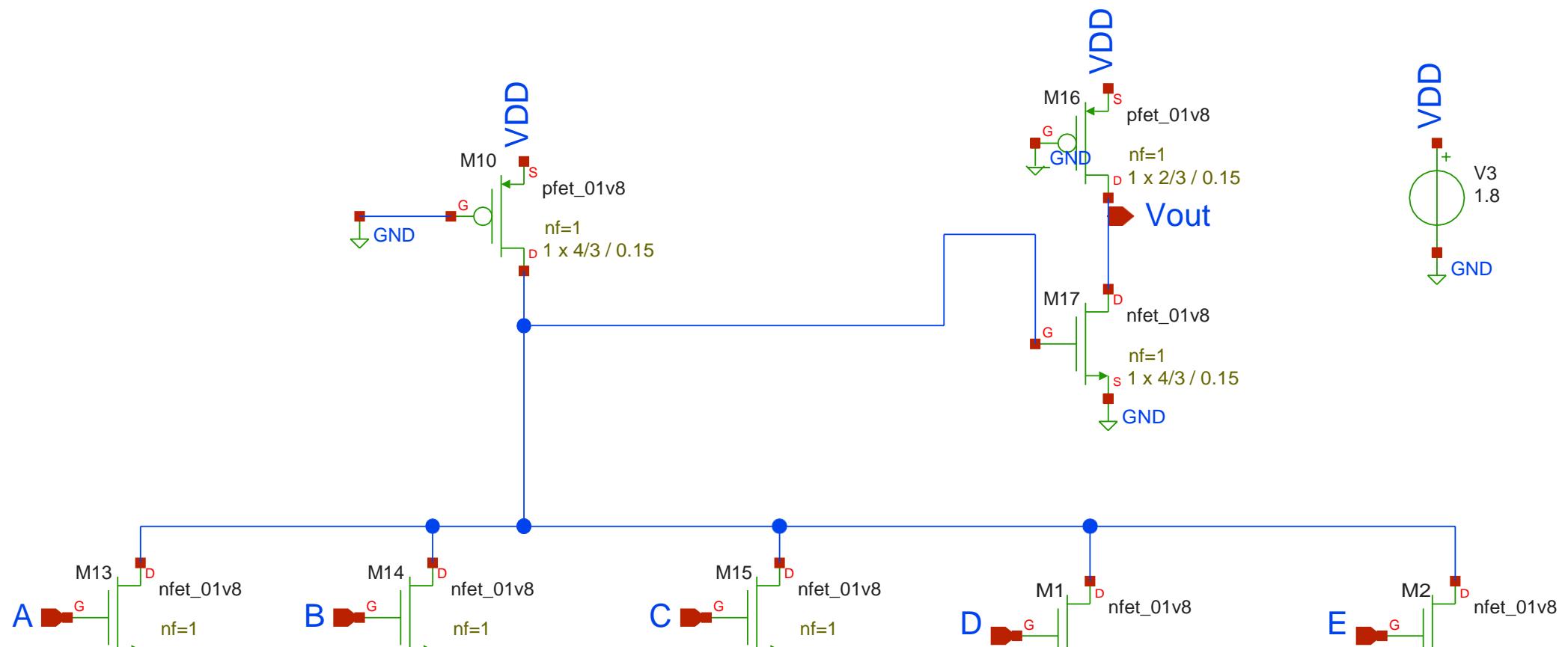

s 1 x 4/3 / 0.15
GND


s 1 x 4/3 / 0.15
____ GND

s 1 x 4/3 / 0.15
____ GND


nf=1
s 1 x 4/3 / 0.15
GND

nf=1
s 1 x 4/3 / 0.15
____ GND

and5.sch

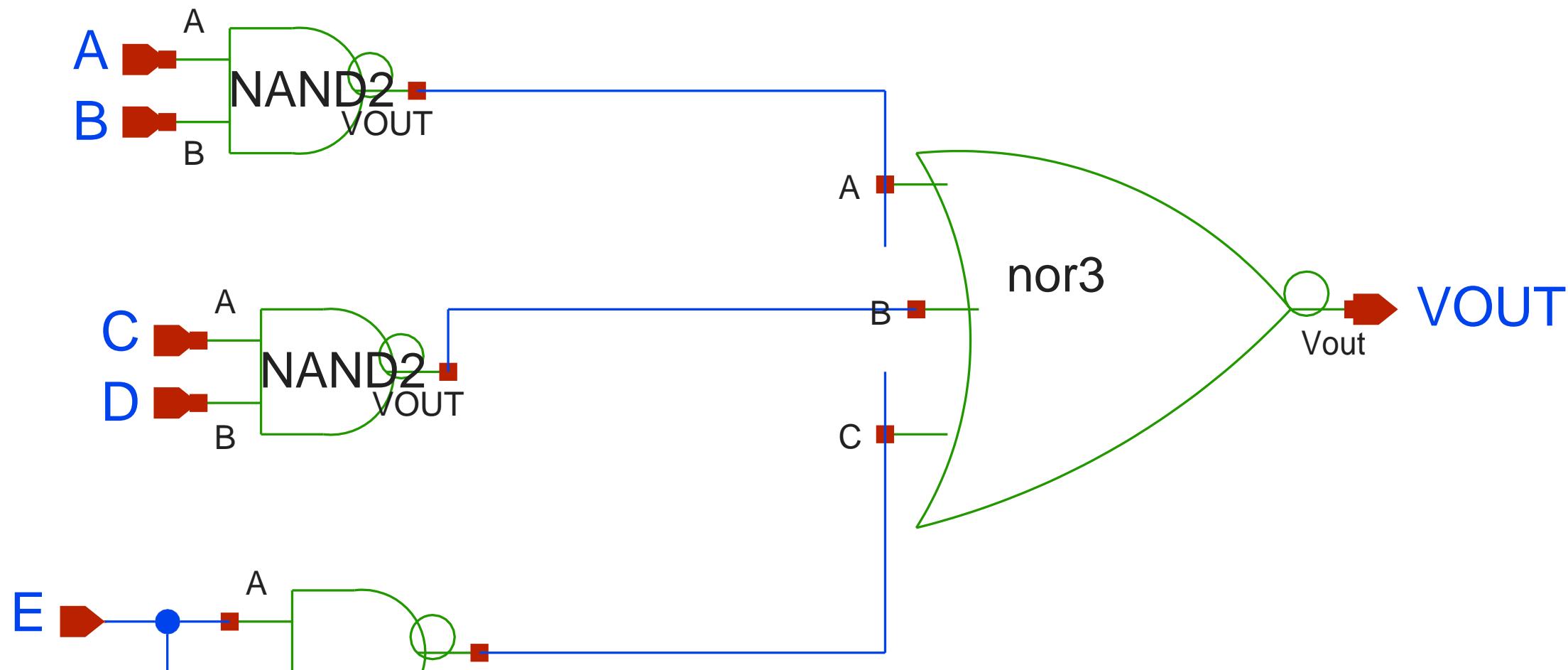



NAND2
VOUT
B

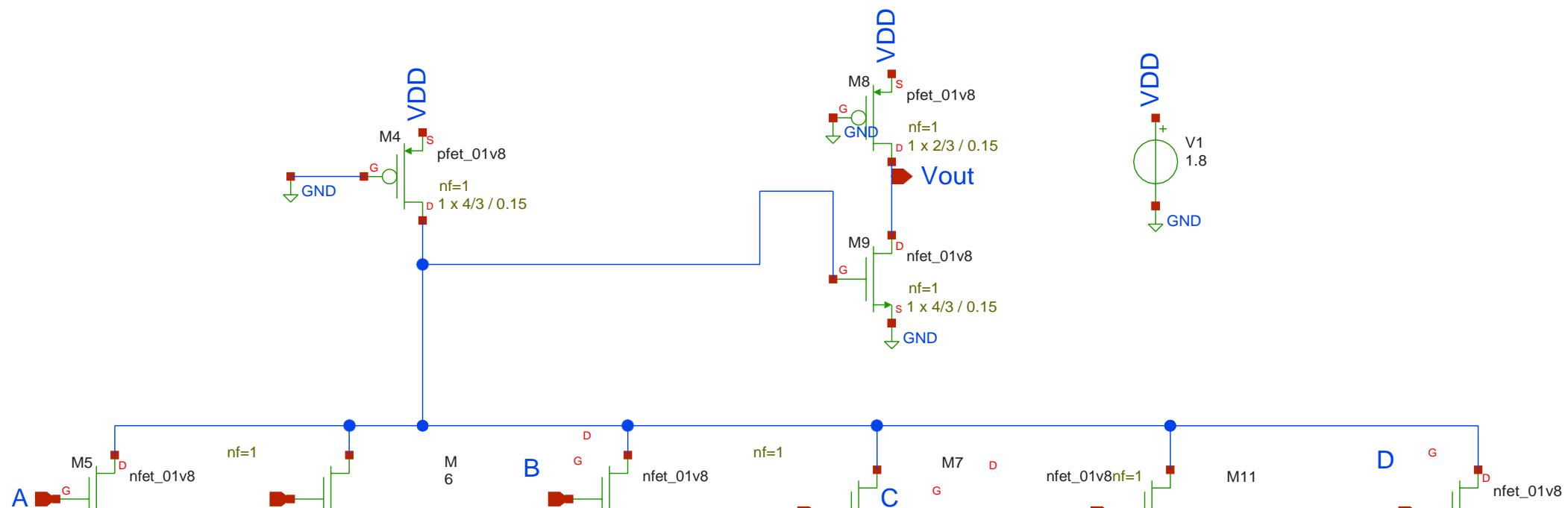



and6.sch

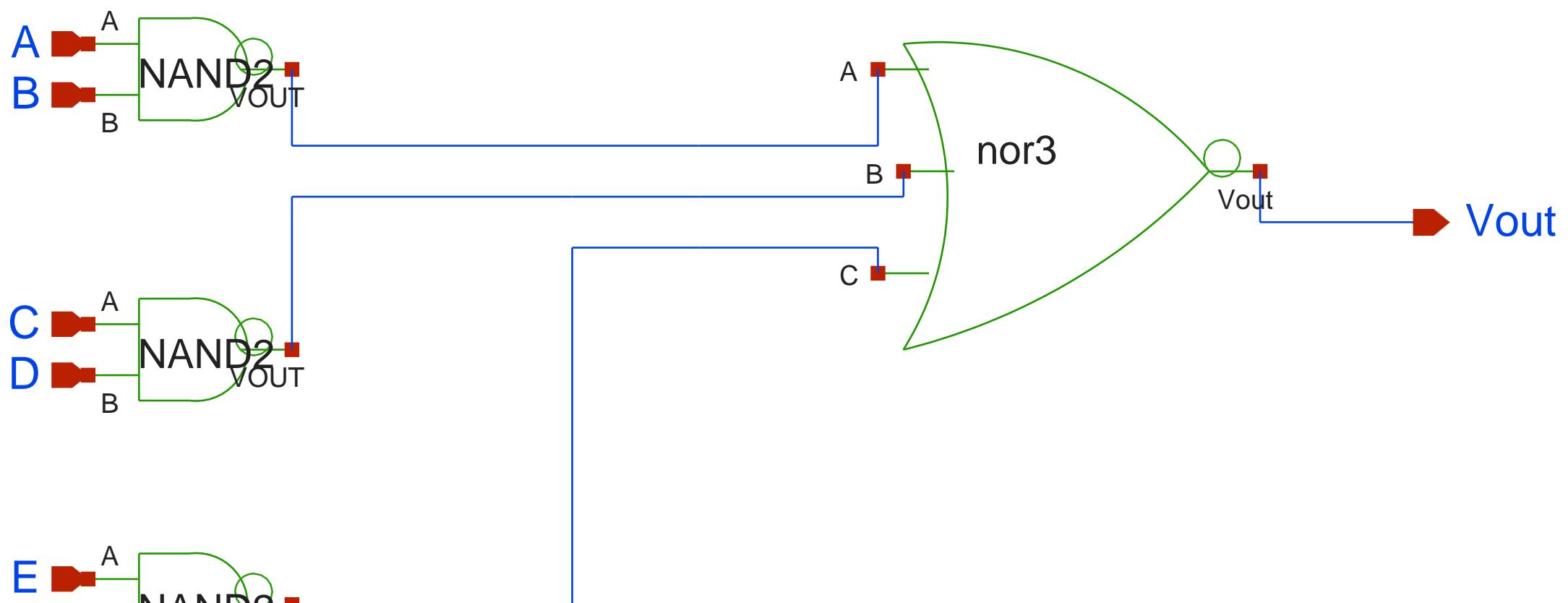

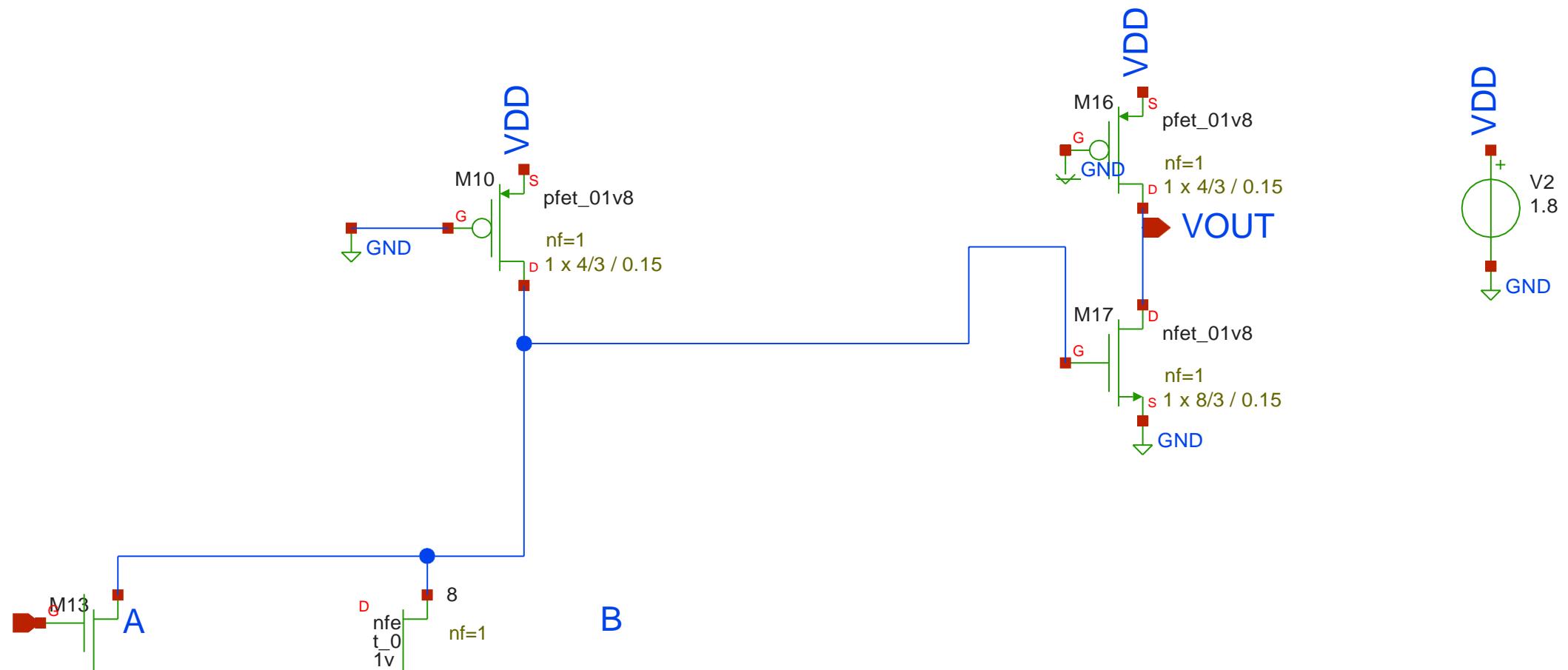

60

s 1 x 8/3 /
0.15



M14

D
nfe
t_0
1v
8

nf
=1
s 1 x
8/3 /
0.15

GND


GND

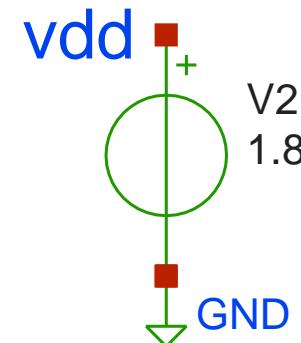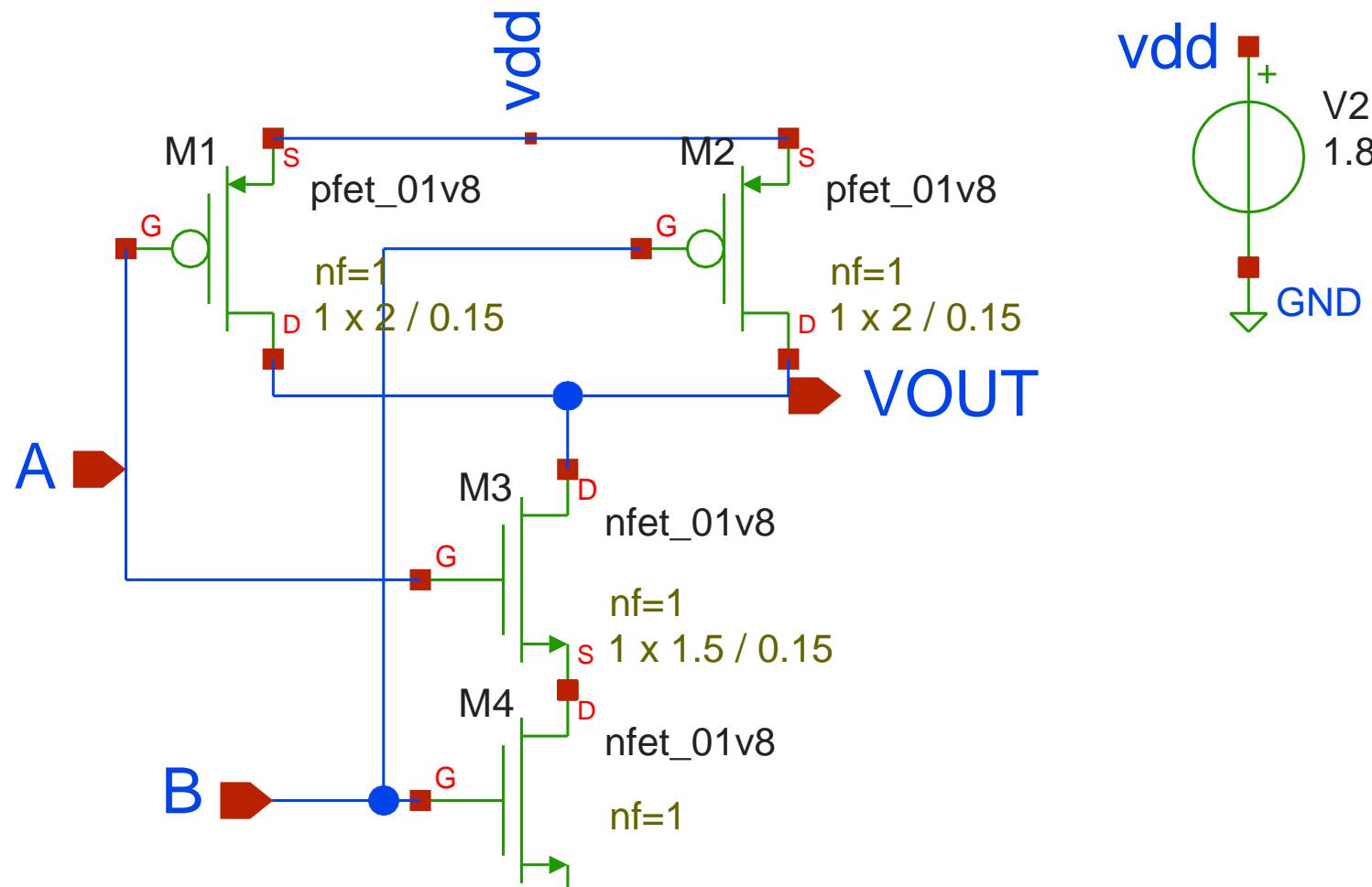

s 1 x 1.5 / 0.15

GND

nand3.sch

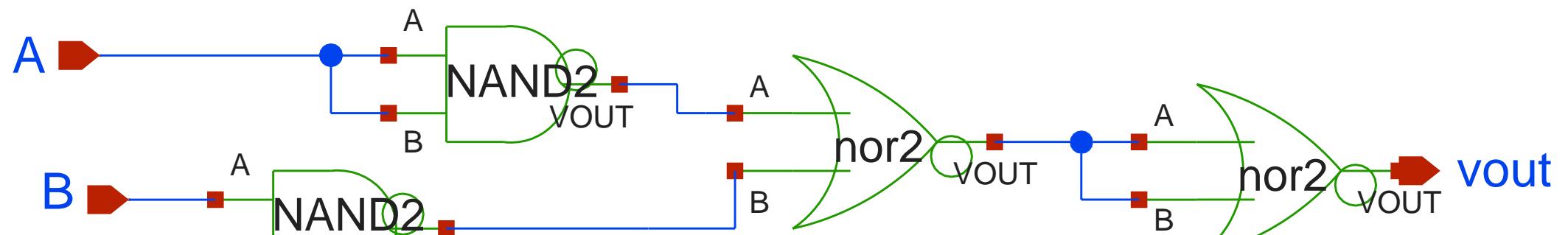

C**B**

VOUT

